

1) a)

000v	00x	00x	0x0	0x0	0x1	0x1	0x1	0x1
001v	0x0	000	1	1	1	1	1	1
010v	x01	001	1	1	1	1	1	1
101v	x10	010	1	1	1	1	1	1
110v	1x1	101	1	1	1	1	1	1
DC 111v	11x	110	1	1	1	1	1	1

$F = \bar{a}b + b\bar{c} + b\bar{c}$

b) 6

a	b	c	10
0	0	1	0
0	1	0	0
1	0	0	0
1	0	1	0


$\bar{F} = a\bar{b}\bar{c} + b\bar{c}$
 $F = a\bar{b}\bar{c} + b\bar{c}$
 $F = \overline{a\bar{b}\bar{c}} \cdot \overline{b\bar{c}}$
 $F = (\bar{a} + b + c)(\bar{b} + \bar{c})$

d) 5

e) It and only if $abc = 0$ in part (a), i.e., the don't-care must not need to change.

2)

Inputs float high.

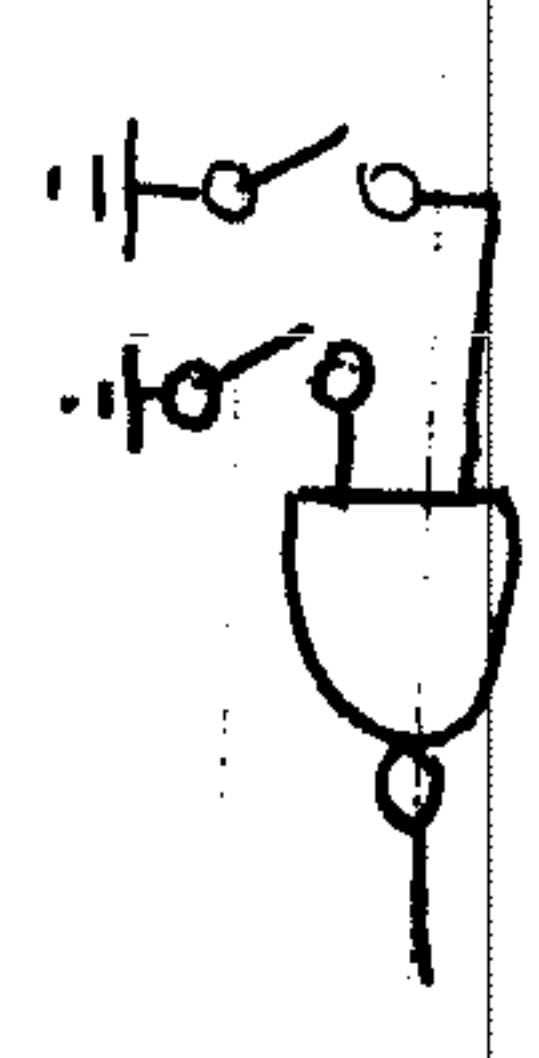

3) a)

0000	0000	0x00
0001	1000	0x10
0010	0100	0x20
0101	1010	0x50
1010	0101	0x95

512	64	8	1
1	2	0	7

1207_8
 647
 $-512 \cdot 1$
 $\hline 135$
 $-64 \cdot 2$
 $\hline 7$
 $-8 \cdot 0$
 $\hline 7$