

EECS 203 Homework 5 Solutions

2.

(a) (10 pts)

Using the codes provided in the assignment, we can create the following Karnaugh maps, and thereby obtain the equations.

A:

L\RE	00	01	11	10
0	0	1	X	0
1	1	X	X	X

Therefore,

$$A = L + E$$

and


B:

L\RE	00	01	11	10
0	0	1	X	1
1	0	X	X	X


$$B = R + E$$

(b) (10 pts)

A 1-input decoder is shown here:

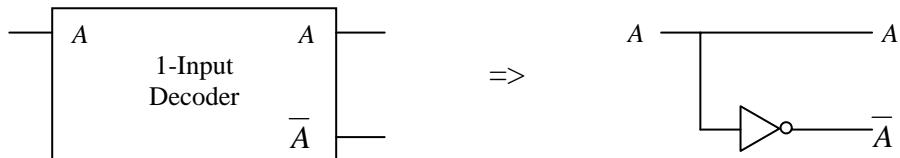

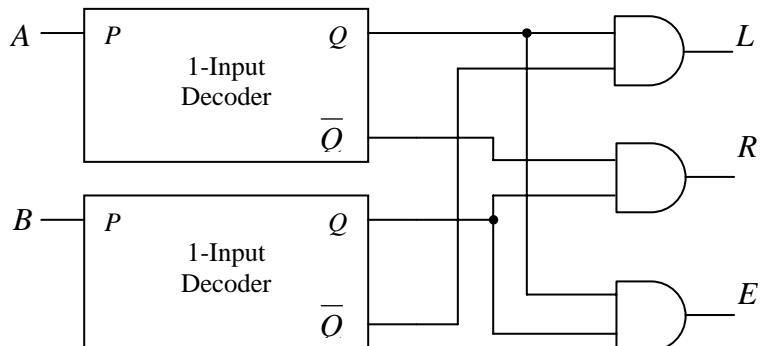
Therefore, using this and some AND gates, we can decode the signals as follows:



(c) i) (10 pts)

Designs can vary.

N: 00  
L: 10  
R: 01  
E: 11

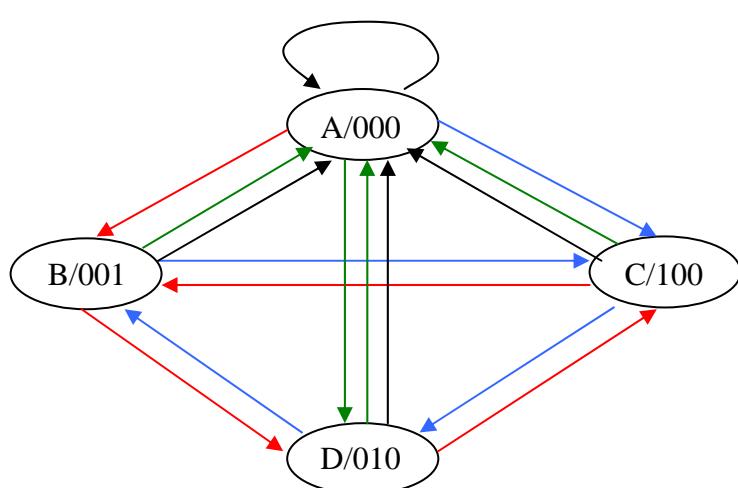

(c) ii) (5 pts)

CS	NS				Output <i>pqr</i>
	<i>i</i> = 00	<i>i</i> = 01	<i>i</i> = 10	<i>i</i> = 11	
A	A	C	B	D	000
B	A	C	D	A	001
C	A	D	B	A	100
D	A	B	C	A	010

(c) iii) (5 pts)

CS	NS ( <i>m'n'</i> )				Output <i>pqr</i>
	<i>i</i> = 00	<i>i</i> = 01	<i>i</i> = 10	<i>i</i> = 11	
A (00)	A (00)	C (10)	B (01)	D (11)	000
B (01)	A (00)	C (10)	D (11)	A (00)	001
C (10)	A (00)	D (11)	B (01)	A (00)	100
D (11)	A (00)	B (01)	C (10)	A (00)	010

(c) iv) (10 pts)

<i>m'</i>	I (ab)			
	00	01	11	10
CS ( <i>mn</i> )	00	0	1	1
	01	0	1	0
	11	0	0	0
	10	0	1	0

<i>n'</i>	i (ab)			
	00	01	11	10
CS ( <i>mn</i> )	00	0	0	1
	01	0	0	1
	11	0	1	0
	10	0	1	1

Therefore, we can solve for the equations as follows

$$m' = \overline{mnb} + \overline{mab} + nab + mnab$$

$$n' = \overline{mna} + \overline{mab} + mab + mnab$$

$$p = mn$$


$$q = mn$$

$$r = \overline{mn}$$


Drawing the circuits should be straightforward using these equations.

4) (10 pts)

Easy solution:

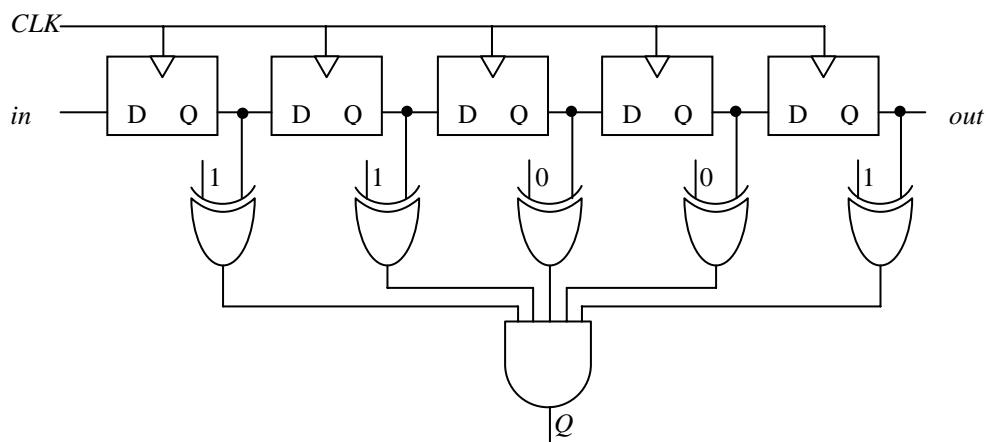

FSM solution:

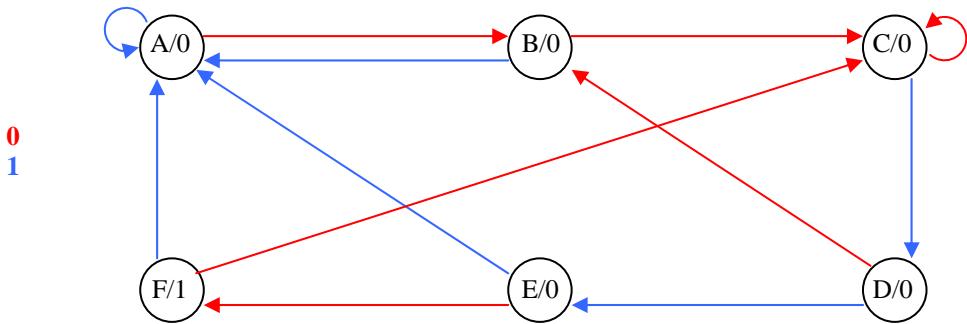

	Next State		
CS	$i=0$	$i=1$	$f$
A	B	A	0
B	C	A	0
C	C	D	0
D	B	E	0
E	F	A	0
F	C	A	1

CS	Next State ( $p'q'r'$ )		
$pqr$	$i=0$	$i=1$	$f$
A (000)	B (110)	A (000)	0
B (110)	C (111)	A (000)	0
C (111)	C (111)	D (001)	0
D (001)	B (110)	E (010)	0
E (010)	F (101)	A (000)	0
F (101)	C (111)	A (000)	1

$p'$	$ri$			
	00	01	11	10
00	1	0	0	1
01	1	0	x	x
11	1	0	0	1
10	x	x	0	1

$q'$	$ri$			
	00	01	11	10
00	1	0	1	0
01	0	0	x	x
11	1	0	0	1
10	x	x	0	1

$r'$	$ri$			
	00	01	11	10
00	0	0	0	0
01	1	0	0	0
11	1	0	1	1
10	x	x	0	1

$$p' = \bar{i}$$

$$q' = \bar{qi} + \bar{pr} + \bar{pi} + \bar{ri}$$

$$r' = \bar{pi} + \bar{qr} + pqr$$

$$f = p\bar{qr}$$

Drawing the circuits should be straightforward using these equations.

5)

- (a) (5 pts) Mealy  
 (b) (4 pts)

Current State	Input	Next State	Output
A	0	D	1
	1	C	1
B	0	A	0
	1	F	0
C	0	C	0
	1	E	1
D	0	C	1
	1	C	1
E	0	B	1
	1	E	1
F	0	A	0
	1	D	1

(c) (5 pts)

CS ( $pqr$ )	Input ( $i$ )	NS ( $p'q'r'$ )	Output ( $z$ )
A (000)	0	D (011)	1
	1	C (010)	1
B (001)	0	A (000)	0
	1	F (101)	0
C (010)	0	C (010)	0
	1	E (100)	1
D (011)	0	C (010)	1
	1	C (010)	1
E (100)	0	B (001)	1
	1	E (100)	1
F (101)	0	A (000)	0
	1	D (011)	1

(d) (10 pts)

$p'$	$ri$					$q'$	$ri$				
	00	01	11	10			00	01	11	10	
$pq$	00	0	0	1	0		00	1	1	0	0
	01	0	1	0	0		01	1	0	1	1
	11	x	x	x	x		11	x	x	x	x
	10	0	1	0	0		10	0	0	1	0

$r'$	$ri$					$z$	$ri$				
	00	01	11	10			00	01	11	10	
$pq$	00	1	0	1	0		00	1	1	0	0
	01	0	0	0	0		01	0	1	1	1
	11	x	x	x	x		11	x	x	x	x
	10	1	0	1	0		10	1	1	1	0

$$p' = \bar{q}ri + \bar{p}ri + \bar{p}\bar{q}ri$$

$$q' = \bar{p}\bar{q}r + \bar{q}r + qr + pri$$

$$r' = \bar{q}ri + \bar{q}ri$$

$$z = \bar{q}r + pi + qi + qr$$

6)

(a) (5 pts)

It is a Moore machine because the outputs depend on the current state, but not the inputs. Although, one output is different for a different input when the current state is A, the output is a don't care, so we can choose it to be 0 and hence make it a Moore machine.

(b) (5 pts)

CS ( $pq$ )	Input ( $i$ )	NS ( $p'q'$ )	Output ( $z$ )
A (00)	0	A (00)	0
	1	C (10)	
B (01)	0	D (11)	0
	1	D (11)	
C (10)	0	A (00)	1
	1	B (01)	
D (11)	0	D (11)	0
	1	C (10)	

$p'$	00	01	11	10
$p \setminus qi$	0	1	1	1
0	0	0	1	1
1	0	0	1	1

$q'$	00	01	11	10
$p \setminus qi$	0	0	0	1
0	0	0	1	1
1	0	1	0	1

$z$	00	01	11	10
$p \setminus qi$	0	0	0	0
0	0	0	0	0
1	1	1	0	0

$$p' = q + \bar{p}i$$

$$q' = \bar{p}q + \bar{q}\bar{i} + p\bar{q}i$$

$$z = p\bar{q}$$