

# Introduction to Computer Engineering – EECS 203

<http://ziyang.eecs.northwestern.edu/~dickrp/eecs203/>

Instructor: Robert Dick  
Office: L477 Tech  
Email: dickrp@northwestern.edu  
Phone: 847-467-2298

TA: Neal Oza  
Office: Tech. Inst. L375  
Phone: 847-467-0033  
Email: nealoza@u.northwestern.edu

TT: David Bild  
Office: Tech. Inst. L470  
Phone: 847-491-2083  
Email: d-bild@northwestern.edu



**NORTHWESTERN**  
**UNIVERSITY**

# Outline

1. Administrative Stuff
2. Review
3. Switch Models
4. Transistors and CMOS Design
5. Homework

# Grading scheme

- 15% homeworks
- 35% labs
- 20% midterm exam
- 30% final exam

## Planned schedule

- Mondays: Labs assigned and collected
- Wednesdays: Homeworks collected and assigned
- Friday's class will normally focus on the lab and homework of the week, and will be given by Neal Oza

# Outline

1. Administrative Stuff
2. Review
3. Switch Models
4. Transistors and CMOS Design
5. Homework


# Review

- What is a truth table?
- Combinational vs. sequential logic?
- Symbol and notation for AND, OR, NOT?
- Other gates also exist, e.g., NAND, NOR, XOR, XNOR

# Case study of simple combinational logic design
 
## Seven-segment display

- Given: A four-bit binary input
- Display a decimal digit ranging from zero to nine
- Use a seven-segment display




## Case study – Seven-segment

$i_3$	$i_2$	$i_1$	$i_0$	dec
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9




## Case study – Seven-segment

 


$i_3$	$i_2$	$i_1$	$i_0$	dec	L1	L2	L3
0	0	0	0	0	1	0	1
0	0	0	1	1	0	0	0
0	0	1	0	2	1	1	1
0	0	1	1	3	1	1	1
0	1	0	0	4	0	1	0
0	1	0	1	5	1	1	1
0	1	1	0	6	1	1	1
0	1	1	1	7	1	0	0
1	0	0	0	8	1	1	1
1	0	0	1	9	1	1	0

# Case study – Seven-segment

 


$i_3$	$i_2$	$i_1$	$i_0$	dec	L1	L2	L3
0	0	0	0	0	1	0	1
0	0	0	1	1	0	0	0
0	0	1	0	2	1	1	1
0	0	1	1	3	1	1	1
0	1	0	0	4	0	1	0
0	1	0	1	5	1	1	1
0	1	1	0	6	1	1	1
0	1	1	1	7	1	0	0
1	0	0	0	8	1	1	1
1	0	0	1	9	1	1	0

# Case study – Seven-segment

 


$i_3$	$i_2$	$i_1$	$i_0$	dec	L1	L2	L3
0	0	0	0	0	1	0	1
0	0	0	1	1	0	0	0
0	0	1	0	2	1	1	1
0	0	1	1	3	1	1	1
0	1	0	0	4	0	1	0
0	1	0	1	5	1	1	1
0	1	1	0	6	1	1	1
0	1	1	1	7	1	0	0
1	0	0	0	8	1	1	1
1	0	0	1	9	1	1	0

## Case study – Seven-segment

 


$i_3$	$i_2$	$i_1$	$i_0$	dec	L1	L2	L3
0	0	0	0	0	1	0	1
0	0	0	1	1	0	0	0
0	0	1	0	2	1	1	1
0	0	1	1	3	1	1	1
0	1	0	0	4	0	1	0
0	1	0	1	5	1	1	1
0	1	1	0	6	1	1	1
0	1	1	1	7	1	0	0
1	0	0	0	8	1	1	1
1	0	0	1	9	1	1	0

# Case study – Seven-segment

 


$i_3$	$i_2$	$i_1$	$i_0$	dec	L1	L2	L3
0	0	0	0	0	1	0	1
0	0	0	1	1	0	0	0
0	0	1	0	2	1	1	1
0	0	1	1	3	1	1	1
0	1	0	0	4	0	1	0
0	1	0	1	5	1	1	1
0	1	1	0	6	1	1	1
0	1	1	1	7	1	0	0
1	0	0	0	8	1	1	1
1	0	0	1	9	1	1	0

## Case study – Seven-segment

 


$i_3$	$i_2$	$i_1$	$i_0$	dec	L1	L2	L3
0	0	0	0	0	1	0	1
0	0	0	1	1	0	0	0
0	0	1	0	2	1	1	1
0	0	1	1	3	1	1	1
0	1	0	0	4	0	1	0
0	1	0	1	5	1	1	1
0	1	1	0	6	1	1	1
0	1	1	1	7	1	0	0
1	0	0	0	8	1	1	1
1	0	0	1	9	1	1	0

## Case study – Seven-segment

 

$i_3$	$i_2$	$i_1$	$i_0$	dec	L1	L2	L3
0	0	0	0	0	1	0	1
0	0	0	1	1	0	0	0
0	0	1	0	2	1	1	1
0	0	1	1	3	1	1	1
0	1	0	0	4	0	1	0
0	1	0	1	5	1	1	1
0	1	1	0	6	1	1	1
0	1	1	1	7	1	0	0
1	0	0	0	8	1	1	1
1	0	0	1	9	1	1	0


# Case study – Seven-segment

 

$i_3$	$i_2$	$i_1$	$i_0$	dec	L1	L2	L3
0	0	0	0	0	1	0	1
0	0	0	1	1	0	0	0
0	0	1	0	2	1	1	1
0	0	1	1	3	1	1	1
0	1	0	0	4	0	1	0
0	1	0	1	5	1	1	1
0	1	1	0	6	1	1	1
0	1	1	1	7	1	0	0
1	0	0	0	8	1	1	1
1	0	0	1	9	1	1	0




# Case study – Seven-segment

 


$i_3$	$i_2$	$i_1$	$i_0$	dec	L1	L2	L3
0	0	0	0	0	1	0	1
0	0	0	1	1	0	0	0
0	0	1	0	2	1	1	1
0	0	1	1	3	1	1	1
0	1	0	0	4	0	1	0
0	1	0	1	5	1	1	1
0	1	1	0	6	1	1	1
0	1	1	1	7	1	0	0
1	0	0	0	8	1	1	1
1	0	0	1	9	1	1	0

## Case study – Seven-segment

 


$i_3$	$i_2$	$i_1$	$i_0$	dec	L1	L2	L3
0	0	0	0	0	1	0	1
0	0	0	1	1	0	0	0
0	0	1	0	2	1	1	1
0	0	1	1	3	1	1	1
0	1	0	0	4	0	1	0
0	1	0	1	5	1	1	1
0	1	1	0	6	1	1	1
0	1	1	1	7	1	0	0
1	0	0	0	8	1	1	1
1	0	0	1	9	1	1	0

# Case study – Seven-segment

 

$i_3$	$i_2$	$i_1$	$i_0$	dec	L1	L2	L3
0	0	0	0	0	1	0	1
0	0	0	1	1	0	0	0
0	0	1	0	2	1	1	1
0	0	1	1	3	1	1	1
0	1	0	0	4	0	1	0
0	1	0	1	5	1	1	1
0	1	1	0	6	1	1	1
0	1	1	1	7	1	0	0
1	0	0	0	8	1	1	1
1	0	0	1	9	1	1	0

## Case study – Seven-segment

 


$i_3$	$i_2$	$i_1$	$i_0$	dec	L1	L2	L3
0	0	0	0	0	1	0	1
0	0	0	1	1	0	0	0
0	0	1	0	2	1	1	1
0	0	1	1	3	1	1	1
0	1	0	0	4	0	1	0
0	1	0	1	5	1	1	1
0	1	1	0	6	1	1	1
0	1	1	1	7	1	0	0
1	0	0	0	8	1	1	1
1	0	0	1	9	1	1	0

# Implement L4

$i_3$	$i_2$	$i_1$	$i_0$	dec	L4
0	0	0	0	0	1
0	0	0	1	1	0
0	0	1	0	2	0
0	0	1	1	3	0
0	1	0	0	4	1
0	1	0	1	5	1
0	1	1	0	6	1
0	1	1	1	7	0
1	0	0	0	8	1
1	0	0	1	9	1

## L4 implementation

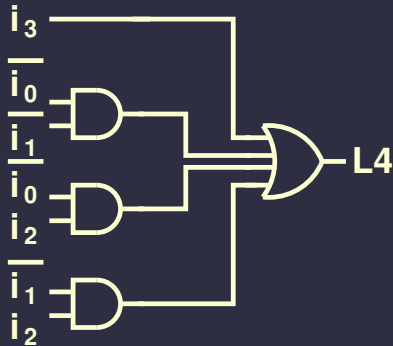

In a future lecture, I'll explain how to do this sort of design.

# Outline

1. Administrative Stuff
2. Review
3. Switch Models
4. Transistors and CMOS Design
5. Homework

# Switch-based design representation







- A switch shorts or opens two points dependant on a control signal
- Used as models for digital transistors
- Why is using normally open and normally closed particularly useful for CMOS?




# Switch-based design representation

- A switch shorts or opens two points dependant on a control signal
- Used as models for digital transistors
- Why is using normally open and normally closed particularly useful for CMOS?
  - NMOS and PMOS transistors easy to model

## Switch-based definitions

      


## Microwave control example

 

- What happens if the cancel button is not pressed and five minutes haven't yet passed?

## Microwave control example

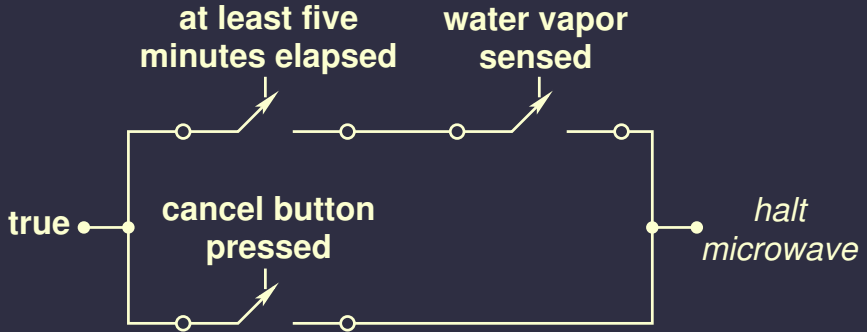


- What happens if the cancel button is not pressed and five minutes haven't yet passed?
  - The output value is undefined.

# Constraints on network output


Under all possible combinations of input values

- Each output must be connected to an input value
- No output may be connected to conflicting input values

## Switch-based *AND*

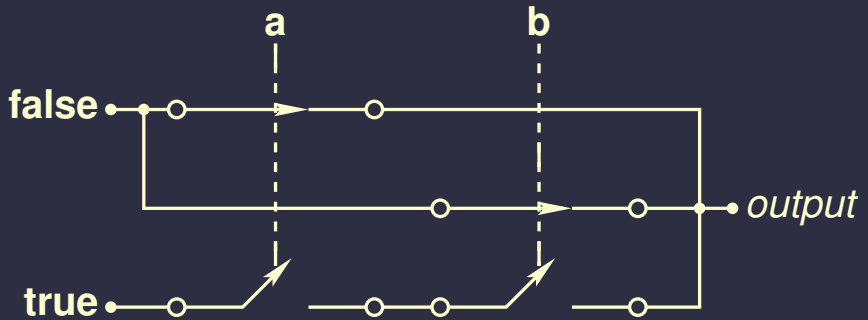

## Switch-based *AND*

 

Note that this requires

- Normally closed switches that transmit false signals well
- Normally open switches that transmit true signals well

# Outline

1. Administrative Stuff
2. Review
3. Switch Models
4. Transistors and CMOS Design
5. Homework



# Relationship with CMOS

- Metal Oxide Semiconductor
- Positive and negative carriers
- Complimentary MOS
- PMOS gates are like normally closed switches that are good at transmitting only true (high) signals
- NMOS gates are like normally open switches that are good at transmitting only false (low) signals

# Relationship with CMOS


- Metal Oxide Semiconductor
- Positive and negative carriers
- Complimentary MOS
- PMOS gates are like normally closed switches that are good at transmitting only true (high) signals
- NMOS gates are like normally open switches that are good at transmitting only false (low) signals

# Relationship with CMOS

- Metal Oxide Semiconductor
- Positive and negative carriers
- Complimentary MOS
- PMOS gates are like normally closed switches that are good at transmitting only true (high) signals
- NMOS gates are like normally open switches that are good at transmitting only false (low) signals
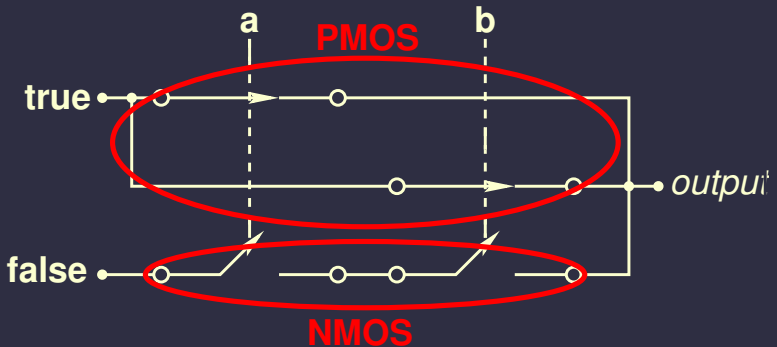
# NAND gate


Therefore, *NAND* and *NOR* gates are used in CMOS design instead of *AND* and *OR* gates



# Transistors

- Basic device in NMOS and PMOS (CMOS) technologies
- Can be used to construct any logic gate

# NMOS transistor

 

# NMOS transistor


- Metal, oxide, semiconductor (MOS)
  - Then it was polysilicon, oxide, semiconductor
  - Now it is metal, hafnium-based low- $k$  dielectric, semiconductor
- P-type bulk silicon doped with positively charged ions
- N-type diffusion regions doped with negatively charged ions
- Gate can be used to pull a few electrons near the oxide
  - Forms channel region, conduction from source to drain starts

# CMOS


- NMOS turns on when the gate is high
- PMOS just like NMOS, with N and P regions swapped
- PMOS turns on when the gate is low
- NMOS good at conducting low (0s)
- PMOS good at conducting high (1s)
- Use NMOS and PMOS transistors together to build circuits
  - Complementary metal oxide silicon (CMOS)




# CMOS NAND gate

 


# CMOS NAND gate

 


# CMOS NAND gate

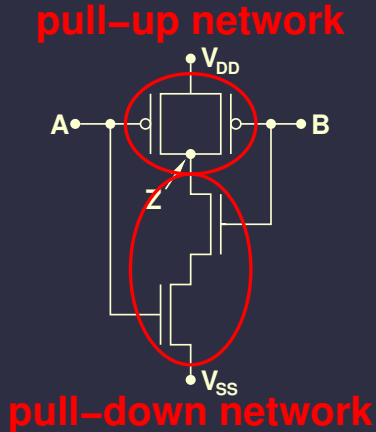


# CMOS NAND gate layout

 


## CMOS inverter operation

 


# CMOS inverter operation

 

# CMOS inverter operation

 


## CMOS inverter operation

 





# CMOS inverter operation

 


## CMOS inverter operation

 


# NAND operation

 


# NAND operation

 


# NAND operation

 


# NAND operation

 

# NAND operation

 


# NAND operation

 





# NAND operation

 


# NAND operation

 


# NOR operation

 


# NOR operation

 


# NOR operation

 


# NOR operation

 

# NOR operation

 


# NOR operation

 




# NOR operation

 

# NOR operation

 

## Section outline

### 4. Transistors and CMOS Design

AND and OR are harder than NAND and NOR

Transmission gates


# NMOS/PMOS transistors for AND/OR

- Recall that NMOS transmits low values easily. . .
- . . . transmits high values poorly
- PMOS transmits high values easily. . .
- . . . transmits low values poorly
- This is due to the effect of the transistors' *threshold* definitions

# NMOS/PMOS transistors for AND/OR

- $V_T$ , or threshold voltage, is commonly 0.7 V
- NMOS conducts when  $V_{GS} > V_T$
- PMOS conducts when  $V_{GS} < -V_T$
- What happens if an NMOS transistor's source is high?
- Or a PMOS transistor's source is low?
- Alternatively, if one states that  $V_{TN} = 0.7$  V and  $V_{TP} = -0.7$  V then NMOS conducts when  $V_{GS} > V_{TN}$  and PMOS conducts when  $V_{GS} < V_{TP}$


# NMOS transistor

 

## NMOS/PMOS transistors for AND/OR


- If an NMOS transistor's input were  $V_{DD}$  (high), for  $V_{GS} > V_{TN}$ , the gate would require a higher voltage than  $V_{DD}$
- If an PMOS transistor's input were  $V_{SS}$  (low), for  $V_{GS} < V_{TP}$ , the gate would require a lower voltage than  $V_{SS}$

# NAND/NOR easy to build in CMOS

 


 
## AND/OR requires more area, power, time



## Section outline


### 4. Transistors and CMOS Design

AND and OR are harder than NAND and NOR  
Transmission gates


# CMOS transmission gates (switches)

- NMOS is good at transmitting 0s
  - Bad at transmitting 1s
- PMOS is good at transmitting 1s
  - Bad at transmitting 0s
- To build a switch, use both: CMOS


# CMOS transmission gate (TG)

 


# CMOS transmission gate (TG)

 


## CMOS transmission gate (TG)

 

## CMOS transmission gate (TG)

 


## CMOS transmission gate (TG)

 





## CMOS transmission gate (TG)

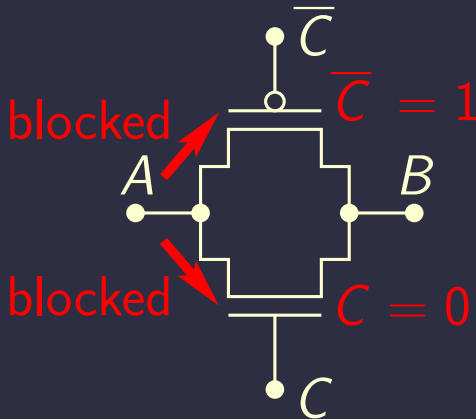



## CMOS transmission gate (TG)

 

## CMOS transmission gate (TG)

 

# Other TG diagram

  

## What can we build with TGs?

- Anything. . . try some examples.

## Computer geek culture reference

- <http://slashdot.org/>
- <http://www.python.org/>

# Outline

1. Administrative Stuff
2. Review
3. Switch Models
4. Transistors and CMOS Design
5. Homework

## Reading assignment

- M. Morris Mano and Charles R. Kime. *Logic and Computer Design Fundamentals*. Prentice-Hall, NJ, fourth edition, 2008
- Sections 2.3–2.5