

Introduction to Computer Engineering – EECS 203

<http://ziyang.eecs.northwestern.edu/~dickrp/eecs203/>

Instructor: Robert Dick
Office: L477 Tech
Email: dickrp@northwestern.edu
Phone: 847-467-2298

TA: Neal Oza
Office: Tech. Inst. L375
Phone: 847-467-0033
Email: nealoza@u.northwestern.edu

TT: David Bild
Office: Tech. Inst. L470
Phone: 847-491-2083
Email: d-bild@northwestern.edu



NORTHWESTERN
UNIVERSITY

Outline

1. Encoders
2. Decoders
3. Multiplexers
4. Homework

Encoders

- Assume you have n one-bit signals
- Only one signal can be 1 at a time
- How many states can you be in?
- How many signals are required to encode all those states?

Encoder example

Pressed (i_2, i_1, i_0)	Code (o_1, o_0)
000	00
001	01
010	10
011	XX
100	11
101	XX
110	XX
111	XX

Implementation?

Priority encoder

What if we want the highest-order high signal to dominate?

<u>Pressed (i_3, i_2, i_1)</u>	<u>Code (o_1, o_0)</u>
000	00
001	01
010	10
011	10
100	11
101	11
110	11
111	11

What impact on implementation efficiency?

Outline

1. Encoders
2. Decoders
3. Multiplexers
4. Homework

Decoders


Need to map back from encoded signal to state

Pressed (i_1, i_0)	Code (o_3, o_2, o_1, o_0)
00	0001
01	0010
10	0100
11	1000


o_0 isn't always used. Why?

Most straightforward implementation?


Straight-forward decoder implementation

 


Straight-forward decoder implementation

 

Straight-forward decoder implementation

 

Straight-forward decoder implementation

 

Decoder implementation efficiency

- n NOTs
- n^2 n -input ANDs
- $\mathcal{O}(n^2)$
- Can't do this for large number of inputs!
- Instead, decompose into multi-level implementation

Multilevel decoder implementation

Starting point

$$o_0 = \overline{i_2} \overline{i_1} \overline{i_0}$$

$$o_1 = \overline{i_2} \overline{i_1} i_0$$

$$o_2 = \overline{i_2} i_1 \overline{i_0}$$

$$o_3 = \overline{i_2} i_1 i_0$$

$$o_4 = i_2 \overline{i_1} \overline{i_0}$$

$$o_5 = i_2 \overline{i_1} i_0$$

$$o_6 = i_2 i_1 \overline{i_0}$$

$$o_7 = i_2 i_1 i_0$$

Multilevel decoder implementation

$$o_0 = \overline{i_2} (\overline{i_1} \overline{i_0})$$

$$o_1 = \overline{i_2} (\overline{i_1} i_0)$$

$$o_2 = \overline{i_2} (i_1 \overline{i_0})$$

$$o_3 = \overline{i_2} (i_1 i_0)$$

$$o_4 = i_2 (\overline{i_1} \overline{i_0})$$

$$o_5 = i_2 (\overline{i_1} i_0)$$

$$o_6 = i_2 (i_1 \overline{i_0})$$

$$o_7 = i_2 (i_1 i_0)$$

Multilevel decoder implementation

$$o_0 = \overline{i_2} (\overline{i_1} \overline{i_0})$$

$$o_1 = \overline{i_2} (\overline{i_1} i_0)$$

$$o_2 = \overline{i_2} (i_1 \overline{i_0})$$

$$o_3 = \overline{i_2} (i_1 i_0)$$

$$o_4 = i_2 (\overline{i_1} \overline{i_0})$$

$$o_5 = i_2 (\overline{i_1} i_0)$$

$$o_6 = i_2 (i_1 \overline{i_0})$$

$$o_7 = i_2 (i_1 i_0)$$

Multilevel decoder implementation

$$o_0 = \overline{i_2} (\overline{i_1} \overline{i_0})$$

$$o_1 = \overline{i_2} (\overline{i_1} i_0)$$

$$o_2 = \overline{i_2} (i_1 \overline{i_0})$$

$$o_3 = \overline{i_2} (i_1 i_0)$$

$$o_4 = i_2 (\overline{i_1} \overline{i_0})$$

$$o_5 = i_2 (\overline{i_1} i_0)$$

$$o_6 = i_2 (i_1 \overline{i_0})$$

$$o_7 = i_2 (i_1 i_0)$$

Reuse terms! Schematic?


Outline

1. Encoders
2. Decoders
3. Multiplexers
4. Homework

Multiplexers or selectors

- Routes one of 2^n inputs to one output
- n control lines
- Can implement with logic gates

Logic gate MUX

 

However, there is another way...


MUX functional table

C	Z
0	I_0
1	I_1



MUX truth table

I_1	I_0	C	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


Review: CMOS transmission gate (TG)

 


Review: Other TG diagram

  


MUX

 


MUX

 


MUX

 


MUX

 


MUX

 



MUX

 


MUX

 


MUX

  


MUX

 


MUX using TGs

 


Hierarchical MUX implementation

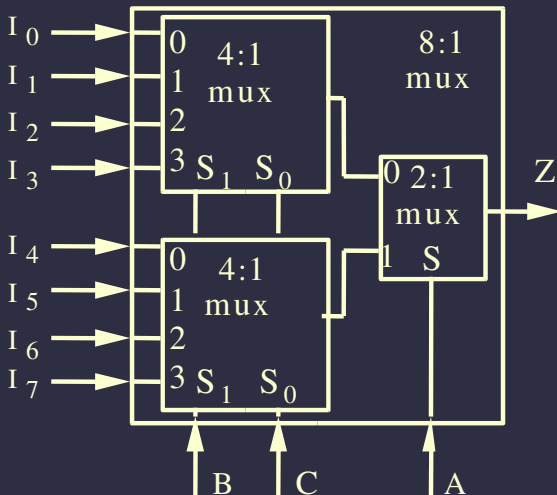

 Alternative hierarchical MUX implementation




MUX examples

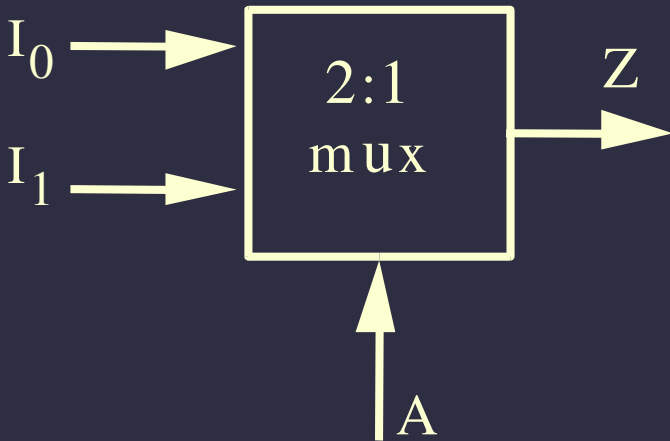


$$Z = \bar{A}I_0 + AI_1$$

MUX examples

 

$$Z = \bar{A}\bar{B}I_0 + \bar{A}BI_1 + A\bar{B}I_2 + ABI_3$$

MUX examples

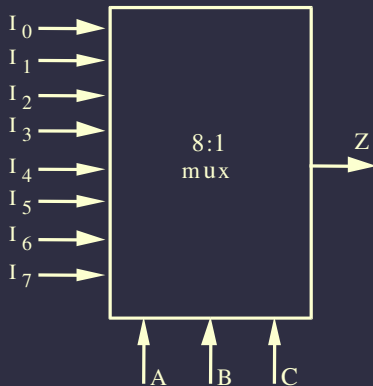

$$Z = \bar{A}\bar{B}\bar{C}I_0 + \bar{A}\bar{B}CI_1 + \bar{A}B\bar{C}I_2 + \bar{A}BCI_3 + \\ AB\bar{C}I_4 + AB\bar{C}I_5 + ABC\bar{C}I_6 + ABCI_7$$

MUX properties

- A $2^n : 1$ MUX can implement any function of n variables
- A $2^{n-1} : 1$ can also be used
 - Use remaining variable as an input to the MUX


MUX example

$$\begin{aligned} F(A, B, C) &= \sum(0, 2, 6, 7) \\ &= \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + AB\overline{C} + ABC \end{aligned}$$

Truth table

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Lookup table implementation

 

MUX example

$$\begin{aligned} F(A, B, C) &= \sum(0, 2, 6, 7) \\ &= \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + AB\overline{C} + ABC \end{aligned}$$

Therefore,

$$\overline{A}\overline{B} \rightarrow F = \overline{C}$$

$$\overline{A}B \rightarrow F = \overline{C}$$

$$A\overline{B} \rightarrow F = 0$$

$$AB \rightarrow F = 1$$

Truth table

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1


$$F = \overline{C}$$

Truth table

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$F = \overline{C}$$


Lookup table implementation

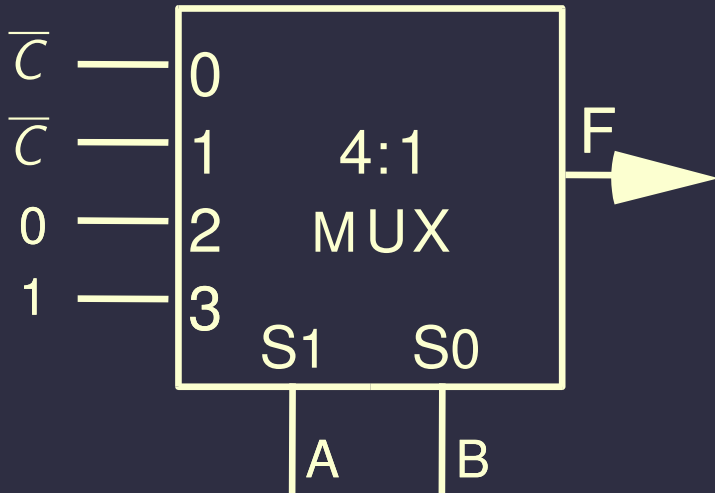


Demultiplexer (DMUX) definitions

- Closely related to *decoders*
- n control signals
- Single data input can be routed to one of 2^n outputs


Recall decoders

 


Recall decoders

 


Recall decoders

 

Recall decoders

 


DMUXs similar to decoders

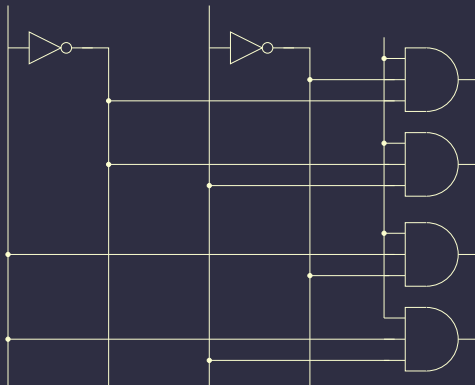


Use extra input to control output signal


Demultiplexer

 


Demultiplexer

 


Demultiplexer

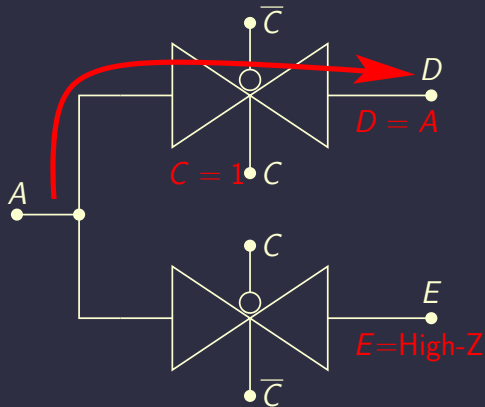


Demultiplexer

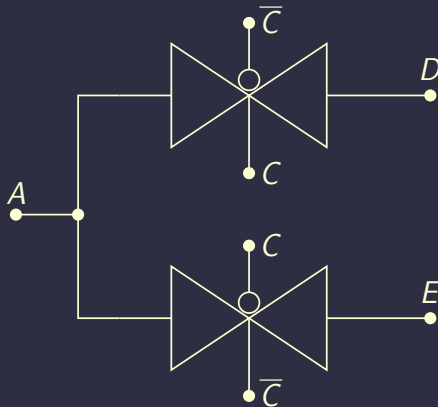


Demultiplexer

 



Demultiplexer

 


Demultiplexer

 


Demultiplexer

  


Demultiplexer

 

Dangers when implementing with TGs

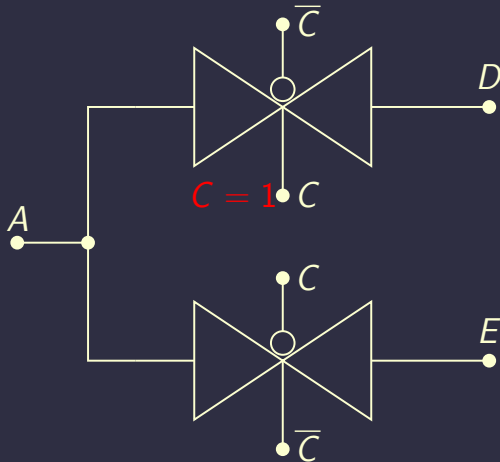


Dangers when implementing with TGs

 


What if an output is not connected to any input?

 Review: Consider undriven inverter inputs



 
Review: Consider undriven inverter inputs




Review: Consider undriven inverter inputs



 
Review: Consider undriven inverter inputs



 
Review: Consider undriven inverter inputs



 
Review: Consider undriven inverter inputs



Set all outputs

 

Demultiplexers as building blocks

 

Generate midterm based on control signals


Example function

$$F_1 = \bar{A}\bar{B}CD + \bar{A}B\bar{C}D + ABCD$$

$$F_2 = AB\bar{C}\bar{D} + ABC = AB\bar{C}\bar{D} + ABC\bar{D} + ABCD$$

$$F_3 = \bar{A} + \bar{B} + \bar{C} + \bar{D} = \overline{ABCD}$$

Demultiplexers as building blocks

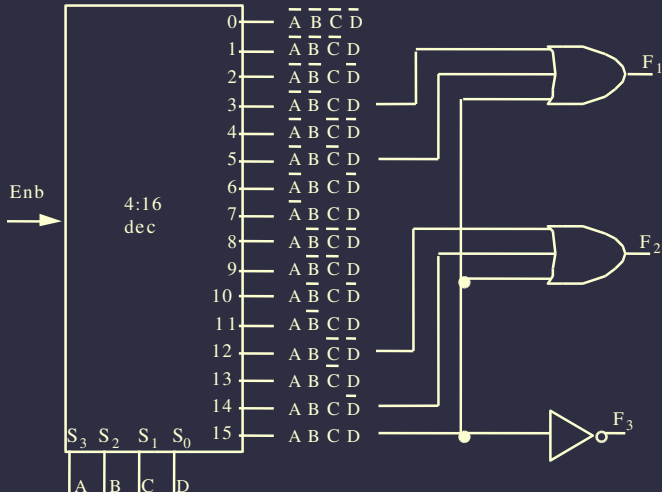

Status

- CMOS
- Switch-based and gate-based design
- Two-level minimization
- Encoders
- Decoder
- Multiplexers
- Demultiplexers

Is anything still unclear? Then let's do some examples!

Lab three

- Requires error detection
- Read Section 1.4 in the book
- How to build an error injector, i.e., a conditional inverter?
- How to build a two-input parity gate?
- How to build a three-input parity gate from two-input parity gates?
- How to detect even number of ones?

Outline

1. Encoders
2. Decoders
3. Multiplexers
4. Homework

Reading assignment

- M. Morris Mano and Charles R. Kime. *Logic and Computer Design Fundamentals*. Prentice-Hall, NJ, fourth edition, 2008
- Sections 1.2–1.7

Computer geek culture reference

- Cliff Stoll. *The Cuckoo's Egg*. Bantam Doubleday Dell Publishing Group, 1989