

Instructor: Robert Dick
 Office: L477 Tech
 Email: dickrp@northwestern.edu
 Phone: 847-467-2298

TA: Neal Oza
 Office: Tech. Inst. L375
 Phone: 847-467-0033
 Email: nealoz@u.northwestern.edu

TT: David Bild
 Office: Tech. Inst. L470
 Phone: 847-491-2083
 Email: d-bild@northwestern.edu



NORTHWESTERN
UNIVERSITY

Boolean algebra

- Set of elements, B
- Binary operators, { [AND, \wedge , $*$, \cdot], [OR, \vee , $+$] }
 - We'll prefer \cdot and $+$
 - \cdot frequently omitted
- Unary operator, [NOT, $'$, $\bar{}$]

Axioms of Boolean algebra

$$\exists x, y \in B \text{ s.t. } x \neq y$$

distributive laws $\forall x, y, z \in B$ $x + (yz) = (x + y)(x + z)$
 $x(y + z) = xy + xz$
 complement $x \in B$ $x\bar{x} = 0$
 $x + \bar{x} = 1$

De Morgan's laws example

$$\overline{a + bc}$$

$$\bar{a} \cdot (\bar{b}\bar{c})$$

$$\bar{a} \cdot (\bar{b} + \bar{c})$$

Quiz (ungraded)

- What is the relationship between a truth table and a Boolean formula? Is it one/many-to-one/many?
- What is the relationship between a Boolean formula and a combinational circuit? Is it one/many-to-one/many?
- What quirks does the CMOS implementation technology have?
- What is signal restoration or voltage regeneration?
- What practices are unsafe in switch-based design? Why?

Axioms of Boolean algebra

$$\exists x, y \in B \text{ s.t. } x \neq y$$

closure $\forall x, y \in B$ $xy \in B$
 $x + y \in B$
 commutative laws $\forall x, y \in B$ $xy = yx$
 $x + y = y + x$
 identities $0, 1 \in B, \forall x \in B$ $x1 = x$
 $x + 0 = x$

De Morgan's laws

$$\overline{(a + b)} = \bar{a}\bar{b}$$

$$\overline{ab} = \bar{a} + \bar{b}$$

$$\overline{f(x_1, x_2, \dots, x_n, \cdot, +)} = f(\bar{x}_1, \bar{x}_2, \dots, \bar{x}_n, +, \cdot)$$

- Those x s could be functions
- Apply in stages
 - Top-down

Representations of Boolean functions

- Truth table
- Expression using only \cdot , $+$, and $'$
- Symbolic
- Karnaugh map
 - More useful as visualization and optimization tool

Review: AND

a	b	a b
0	0	0
0	1	0
1	0	0
1	1	1



$a \text{ AND } b = a b$
Will show Karnaugh map later

Review: OR

a	b	a + b
0	0	0
0	1	1
1	0	1
1	1	1



$a \text{ OR } b = a + b$


Review: NOT

a	\bar{a}
0	1
1	0




$\text{NOT } a = \bar{a}$

Different representations possible

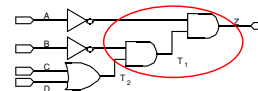

$$Z = ((C + D)\bar{B})\bar{A}$$

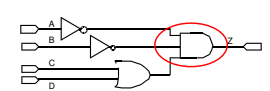

$$Z = (C + D)\bar{A}B$$

Simplifying logic functions

- Minimize literal count (related to gate count, delay)
- Minimize gate count
- Minimize levels (delay)
- Trade off delay for area
 - Sometimes no real cost

Proving theorems = simplification

Prove $XY + X\bar{Y} = X$

$$XY + X\bar{Y} = X(Y + \bar{Y})$$

distributive law

$$X(Y + \bar{Y}) = X(1)$$

complementary law

$$X(1) = X$$

identity law

Proving theorems = simplification

Prove $X + XY = X$

$$X + XY = X1 + XY$$

identity law

$$X1 + XY = X(1 + Y)$$

distributive law

$$X(1 + Y) = X1$$

identity law



$$X1 = X$$

identity law

Literals

- Each appearance of a variable (complement) in expression
- Fewer literals usually implies simpler to implement
- E.g., $Z = \bar{A}\bar{B}C + \bar{A}B + \bar{A}\bar{B}\bar{C} + \bar{B}C$
 - Three variables, ten literals

NANDs and NORs

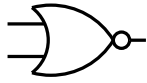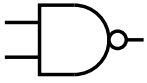

- Can be implemented in CMOS
 - More on this later
- $X \text{ NAND } Y = \overline{XY}$
- $X \text{ NOR } Y = \overline{X + Y}$
- Do we need inverters?

Reading assignment

- M. Morris Mano and Charles R. Kime. *Logic and Computer Design Fundamentals*. Prentice-Hall, NJ, fourth edition, 2008
- Sections 2.4 and 2.5

Summary

- Administrative details
- Finished CMOS and basic gates
- Boolean algebra

Next lectures

- Karnaugh maps
- Visual minimization
- We'll also learn the optimal Quine-McCluskey method
 - Optimal two-level minimization is fun!