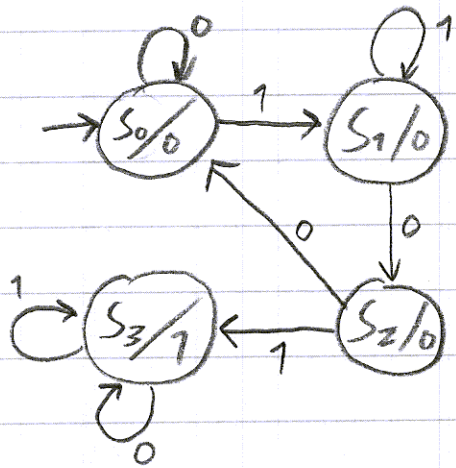


Robert Dick

EECS 303 Final

6 Dec. 2006

1.2)




1.1)

	NS(i)			
CS	0	1		Z
S ₀	S ₀	S ₁		0
S ₁	S ₂	S ₁		0
S ₂	S ₀	S ₃		0
S ₃	S ₃	S ₃		1

1.3) $(0+1)^* 1 0 1 (0+1)^*$

2)

B	BD BC			
C	AC	AB		
D	AD	AB	CD	
E	AE DE AC	AB	BE	1
	A	B	C	D

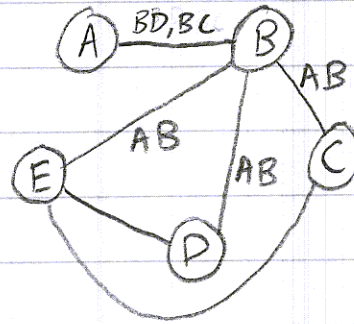

BE

Prime compat.

$BDE \rightarrow AB$

DE

$AB \rightarrow BD, BC$

$BC \rightarrow AB$

$CE \rightarrow BE$

A

B


C

	α BDE	β DE	γ AB	BC	CE	A	B	C
A			1			1		
B	1		1	1			1	
C				1	1			1
D	1	1						
E	1	1			1			
BDE	0		1					
AB			0	1				
BD, BC	1							
CE	1				0			
BE								

Best case is 3, even if implications neglected.

2)

	NS(i)		
CS	0	1	Z
β	α	γ	0
α	α	β	0
γ	γ	β	1

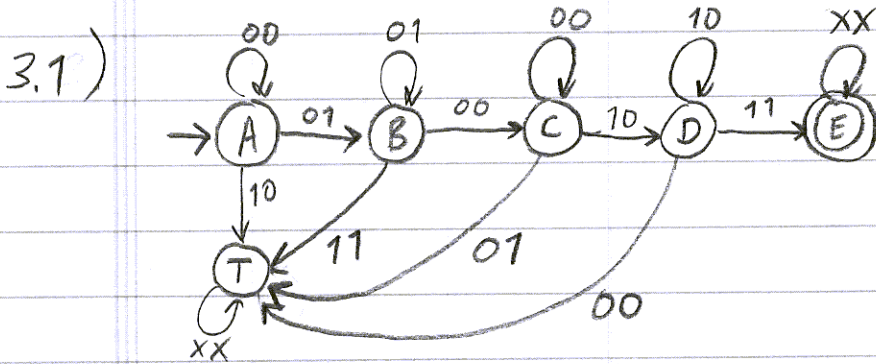

Four adj. to T. Need 4 state variables before state splitting. However, using multiple T states permits 3 variables.

	A	B	C	T ₂
P	X	T ₁	D	E

	NS($\alpha \beta$)				
CS	00	01	10	11	Z
A(000)	A(000)	B(001)	T ₂ (010)	X	0
B(001)	C(011)	B(001)	X	T ₁ (101)	0
C(011)	C(011)	D(111)	T ₂ (010)	X	0
D(111)	T ₁ (101)	D(111)	X	E(110)	0
E(110)	E(110)	"	"	E(110)	1
T ₁ (101)	T ₁ (101)	"	"	"	0
T ₂ (010)	T ₂ (010)	"	"	"	0

3.2) Without a clock signal, f^+ and f cannot be distinguished.

3.3) Kernel extraction could introduce dynamic hazards, resulting in incorrect transitions. Using it would therefore be dangerous.

4) Only sum of odd and even is odd.

$$s_0 = a_0 \oplus b_0$$

$$s_1 = a_1 \oplus b_1 \oplus (a_0 b_0)$$

$$s_2 = a_1 b_1 + a_1 (a_0 b_0) + b_1 (a_0 b_0)$$

$$s_0 = \bar{a}_0 b_0 + a_0 \bar{b}_0, \quad s_2 = a_1 b_1 + a_1 a_0 b_0 + b_1 a_0 b_0$$

$$s_1 = (\bar{a}_1 b_1 + a_1 \bar{b}_1) \oplus (a_0 b_0)$$


$$s_1 = \overline{\bar{a}_1 b_1 + a_1 \bar{b}_1} \cdot a_0 b_0 + (\bar{a}_1 b_1 + a_1 \bar{b}_1) \overline{a_0 b_0}$$

$$s_1 = \bar{a}_1 \bar{b}_1 \cdot \overline{a_1 b_1} \cdot a_0 b_0 + (\bar{a}_1 b_1 + a_1 \bar{b}_1) (\bar{a}_0 + \bar{b}_0)$$


$$s_1 = (a_1 + \bar{b}_1) (\bar{a}_1 + b_1) a_0 b_0 + \bar{a}_0 \bar{a}_1 b_1 + \bar{a}_0 a_1 \bar{b}_1 + \bar{a}_1 \bar{b}_0 b_1 + a_1 \bar{b}_0 \bar{b}_1$$

$$s_1 = (\bar{a}_1 \bar{a}_1 + a_1 b_1 + \bar{b}_1 \bar{a}_1 + \bar{b}_1 b_1) a_0 b_0 + \bar{a}_0 \bar{a}_1 b_1 + \bar{a}_0 a_1 \bar{b}_1 + \bar{a}_1 \bar{b}_0 b_1 + a_1 \bar{b}_0 \bar{b}_1$$
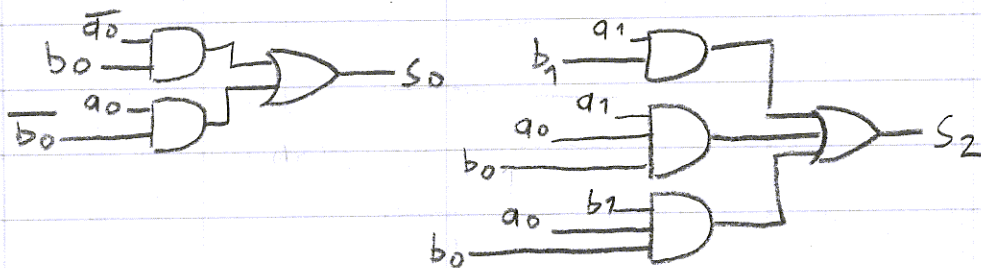
$$s_1 = a_1 b_1 a_0 b_0 + \bar{a}_1 \bar{b}_1 a_0 b_0 + \bar{a}_0 \bar{a}_1 b_1 + \bar{a}_0 a_1 \bar{b}_1 + \bar{b}_0 \bar{a}_1 b_1 + \bar{b}_0 a_1 \bar{b}_1$$



4)



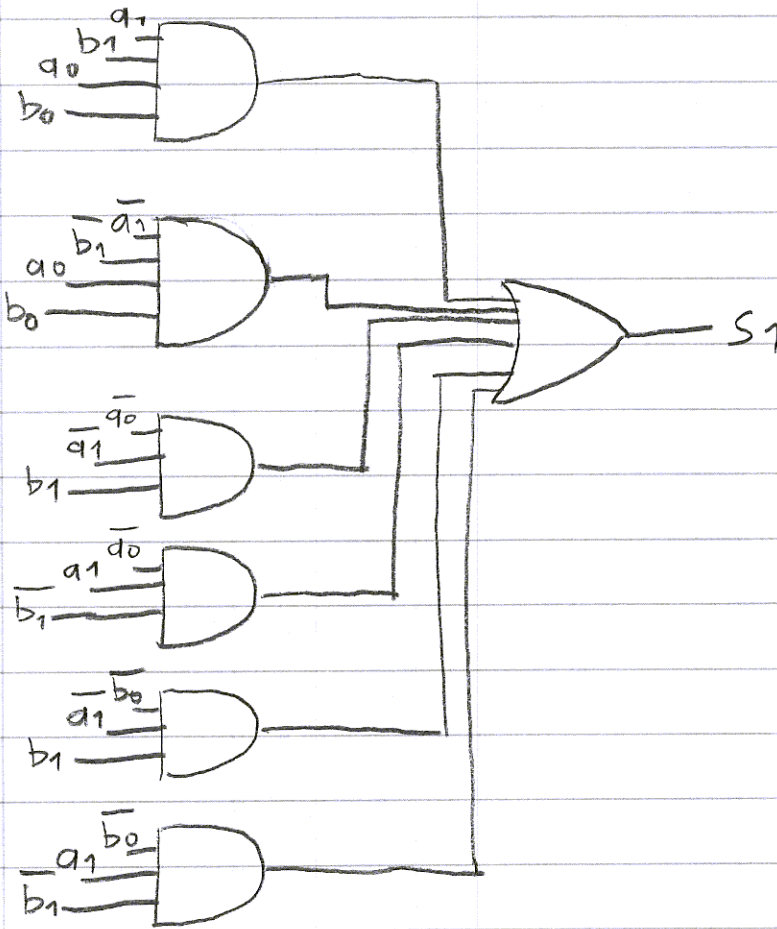


5.1)

	bc			
a	1	1	0	1
	0	0	0	0

$$f_1 = \bar{a}\bar{b} + \bar{a}\bar{c}$$

$$f_2 = (\bar{a})(\bar{b} + \bar{c})$$

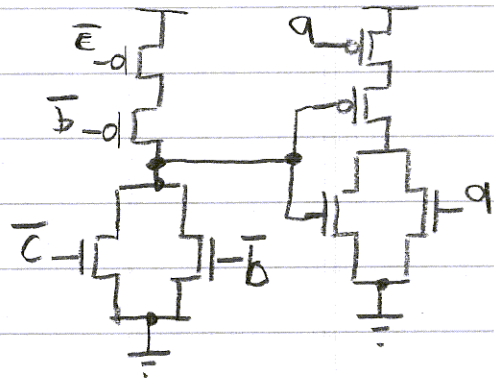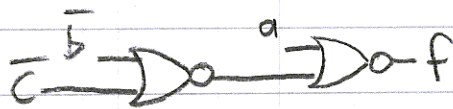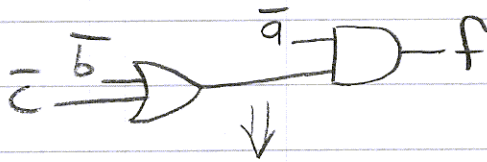


5.2) 8

6) Which states can be reached from A in M_1 and M_2 ?

$M_1: A, D, E, C \rightarrow A, C, D, E$

$M_2: A, B, D, E, F, C \rightarrow A, B, C, D, E, F$

Minimize


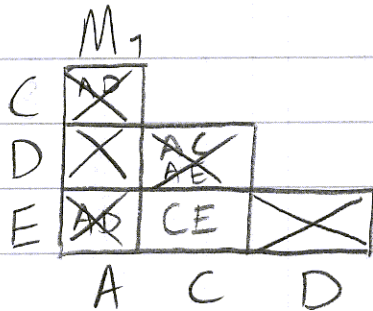


Merge CE

	NS(i)		
CS	0	1	Z
A	D	CE	0
D	CE	A	1
CE	A	CE	0

↓

CS	0	1	Z
α	β	γ	0
β	γ	α	1
γ	α	γ	0

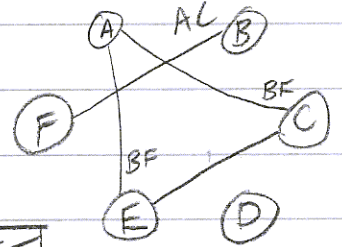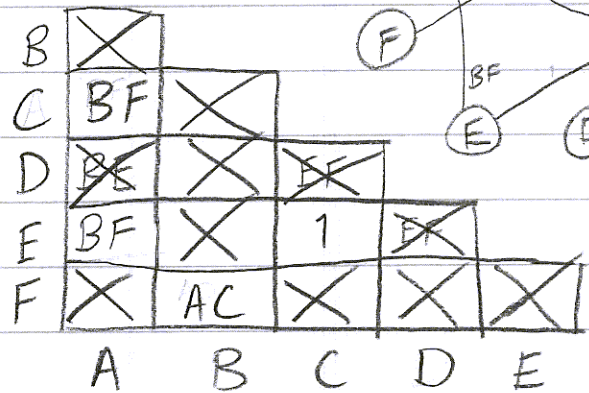

$ACE \rightarrow BF$

CE

$BF \rightarrow AC$

A

D

B

F

6)

	ACE	CE	BF	A	D	B	F
A	1			1			
B			1			1	
C	1	1					
D					1		
E	1	1					
F			1				1
ACE \rightarrow BF	0		1				
BF \rightarrow AC	1		0				

Best case would require 3 states,
even w/o. implications.

	NS(i)		
CS	0	1	Z
ACE	BF	D	0
BF	D	ACE	1
D	ACE	D	0
	↓		
CS	0	1	Z
α	β	γ	0
β	γ	α	1
γ	α	γ	0

Equiv.