

Advanced Digital Logic Design – EECS 303

<http://ziyang.eecs.northwestern.edu/eecs303/>

Teacher: Robert Dick
Office: L477 Tech
Email: dickrp@northwestern.edu
Phone: 847-467-2298



NORTHWESTERN
UNIVERSITY

Outline

1. Multilevel minimization
2. Timing

Section outline

1. Multilevel minimization

Examples

Ad-hoc method


Kernel extraction

Multi-level example


- So far, we have talked about two-level logic
 - Fewest number of levels that is fully general
- However, there are some circuits that can more efficiently be implemented using three or more levels
- Even basic functions, like NANDS and NORS, are commonly composed of multiple gates if the fan-in is high

Two-level form
 
$$X(A, B, C, D, E, F, G) = ADF + AEF + BDF + BEF + CDF + CEF + G$$



Two-level form

 


- 6 × 3-input AND gates
- 1 × 7-input OR gate (may not exist!)
- 25 wires (19 literals plus 6 internal wires)


Multi-level form

Factor:
 
$$\begin{aligned} X(A, B, C, D, E, F, G) &= ADF + AEF + BDF + BEF + \\ & CDF + CEF + G \\ &= (A + B + C)(D + E)F + G \end{aligned}$$




Multi-level form

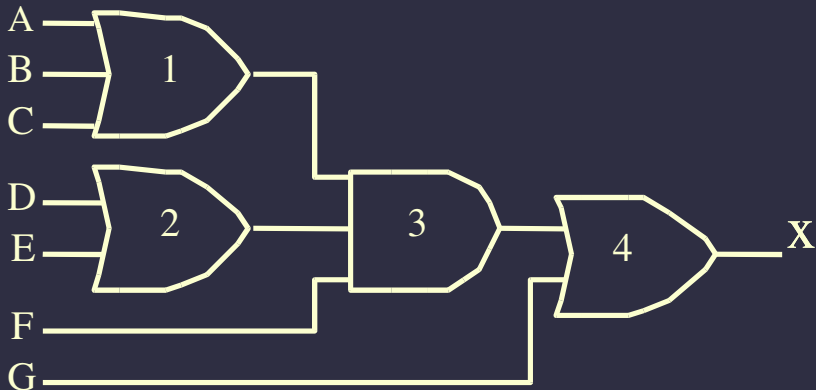


- 1 × 3-input OR gate, 2 × 2-input OR gates
- 1 × 3-input AND gate
- 10 wires (7 literals plus 3 internal wires)


Multi-level implementation of NAND8

 



Multi-level implementation of NAND8

 


Multi-level implementation of NAND8

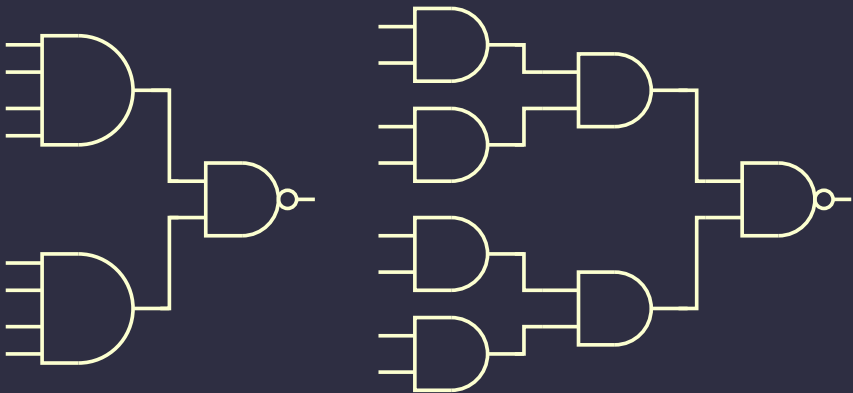

Multi-level implementation of NAND8

  

Multi-level implementation of NAND8

 

Convert middle ANDs to NORs with inverted inputs


Multi-level logic

$$F = A (B + C D) + B$$


**Original
AND-OR Network**



 
**Introduction and
Conservation of Bubbles**



 
**Redrawn in terms
of conventional
NAND Gates**




Multi-level logic

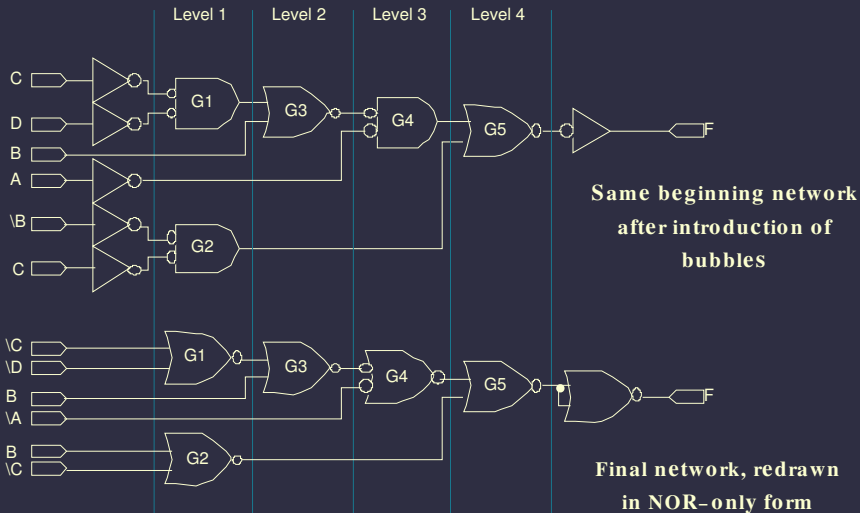


NAND/NOR conversion for uneven paths

 


Original circuit

 

Add double bubbles at inputs

 

**Distribute bubbles
some mismatches**

 

Insert inverters to fix mismatches

Section outline

1. Multilevel minimization

Examples

Ad-hoc method

Kernel extraction

Multi-level minimization objectives

- Factor out common sub-logic (reduce fan-in, increase gate levels), subject to timing constraints
- Map factored form onto library of gates
- Minimize number of literals (correlates with number of wires)

$$X = (AB + \bar{B}C)(C + D(E + \bar{A}\bar{C})) + (D + E)(FG)$$

Multi-level minimization

Can interactively apply the following operations

- Decomposition
- Extraction
- Factoring
- Substitution
- Collapsing

Multi-level minimization

- Recall that two-level minimization is difficult
 - Quine-McCluskey is too slow for large problems
 - Resort to potentially sub-optimal heuristic
 - Espresso
- Multi-level minimization is much harder
 - No known efficient algorithm gives optimal solution
 - MIS uses heuristics to usually produce good solutions

Decomposition

Take a single Boolean expression and replace it with a collection of new expressions

$$L = ABC + ABD + \bar{A} \bar{C} \bar{D} + \bar{B} \bar{C} \bar{D} \quad 12 \text{ literals}$$

L rewritten as

$$L = MN + \bar{M} \bar{N} \quad 8 \text{ literals}$$

$$M = AB$$

$$N = C + D$$

Decomposition

$$L = ABC + ABD + \bar{A} \bar{C} \bar{D} + \bar{B} \bar{C} \bar{D}$$

$$= AB(C + D) + (\bar{A} + \bar{B})\bar{C} \bar{D}$$


$$= AB(C + D) + \overline{(\bar{A}\bar{B})} \overline{(\bar{C}\bar{D})}$$

$$M = AB$$


$$N = C + D$$

$$L = MN + \bar{M} \bar{N}$$

Decomposition

 

Before Decomposition

 

After Decomposition

Extraction

- Extraction is decomposition applied to multiple functions
- The best decomposition for a single function may not be the best if there are multiple outputs
- Ideally, extracted sub-function can be re-used in producing many outputs

Extraction

$$L = (A + B)CD + E \quad 11 \text{ literals}$$

$$M = (A + B)\bar{E}$$

$$N = CDE$$

Can be re-written as

$$L = XY + E \quad 11 \text{ literals}$$


$$M = X\bar{E}$$

$$N = YE$$


$$X = A + B$$

$$Y = CD$$

Extraction

 

Before Extraction

 

After Extraction

Gate count has improved, literals is unchanged

Extraction example

Given equations of a Boolean Network

$$L = AF + BF + AG + CG + ADE + BDE + CDE \quad 33 \text{ literals}$$

$$M = AF + BF + ACE + BCE$$

$$N = ADE + CDE$$

Find the best kernel of these functions. If the kernel is $(A + B)$, then

$$L = DEM + FP + AG + CG \quad 22 \text{ literals}$$

$$M = CEP + FP$$

$$N = ADE + CDE$$

$$P = A + B$$

Cube extraction

Can restrict divisors to single cubes

$$L = ABC + ABD + EG \quad 16 \text{ literals}$$

$$M = ABFG$$

$$N = BD + EF$$

We can obtain the best cube AB to divide the functions

$$L = PC + PD + EG \quad 15 \text{ literals}$$

$$M = PFG$$

$$N = BD + EF$$

$$P = AB$$

Factoring


Expression in two-level form re-expressed in multi-level form without introducing intermediate functions

$$L = AC + AD + BC + BD + E \quad 9 \text{ literals}$$


Can be rewritten as

$$L = (A + B)(C + D) + E \quad 5 \text{ literals}$$

Factoring

 

Before Factoring

 

After Factoring

Substitution

Express L in terms of M

$$L = A + BC$$

5 literals

$$M = A + B$$

L rewritten in terms of M

$$L = M(A + C)$$

5 literals

$$M = A + B$$

Collapsing

Reverse of substitution. Sometimes eliminates levels to meet timing constraints.

$$L = M(A + C)$$

5 literals

$$M = A + B$$

only 2 additional

$$\begin{aligned} L &= (A + B)(A + C) \\ &= AA + AC + AB + BC \\ &= A + BC \end{aligned}$$

Redundancy

- Minimizing gate count and literals isn't always good for performance or power consumption
- Using redundant sub-circuits can result in improvements
- The wiring required to re-use sub-functions can result in larger delays than redundant sub-functions

Boolean division

$$L = PQ + R$$

P divisor

Q quotient

R remainder

$$X = AC + AD + BC + BD + E$$

$$Y = A + B$$

X divided by Y expressed as

$$X = Y(C + D) + E$$

P and Q are symmetrical

Boolean division

Finding divisors that lead greatest number of common subexpressions is difficult

$$L = AD + BCD + E$$

$$M = A + B$$

M does not divide L under algebraic division rules

M does divide L under Boolean rules (very large number of these!)

$$L/M = (A + C)D$$

Boolean division

$$L = AD + BCD + E$$

$$M = A + B$$

$$\begin{aligned} L &= (A + B)(AD + CD) + E \\ &= (A + B)(A + C)D + E \end{aligned}$$

Boolean division

This follows from writing L in $MQ + R$ form

$$\begin{aligned}L &= M((A + C)D) + E \\ &= (A + B)(A + C)D + E \\ &= (AA + AC + AB + BC)D + E \\ &= (A + BC)D + E \\ &= AD + BCD + E\end{aligned}$$

Section outline

1. Multilevel minimization

Examples

Ad-hoc method

Kernel extraction

Multi-level minimization definitions

- A variable is a symbol representing a single coordinate in a Boolean space, e.g., A or B
- Literal is a variable or its negation, e.g., A or \bar{A}
- A cube, C , is a set of literals, e.g., $A B \bar{C}$ or $A \bar{B}$
- Consider a sum-of-products expression

$$L = AF + BF + AG + CG + ADE + BDE + CDE$$

- The primary divisors of an expression form a set of expressions

$$D(L) = \{L/C \mid C \text{ is a cube}\}$$

Multi-level minimization definitions

- Equation is cube-free if no cubes divide it evenly
- $AB + C$ is cube-free
- $AB + AC$ is not cube-free
 - Divided evenly by A

Multi-level minimization definitions

- The kernels of an expression are sets of expressions

$$K(L) = \{G \mid G \in D(L) \text{ and } G \text{ is cube-free}\}$$

- In other words, the kernels are divisors of the function for cube quotients that can not be evenly divided (remainder-free) by other cubes
- The cube C used to divide L to obtain the kernel $K(L)$ is called the co-kernel

Kernel

$$L = AF + BF + AG + CG + ADE + BDE + CDE$$

Cube	Primary divisor	Kernel (cube free)
A	$(F + G + DE)$	k_1
B	$(F + DE)$	k_2
C	$(G + DE)$	k_3
D	$(AE + BE + CE)$	no
E	$(AD + BD + CD)$	no
F	$(A + B)$	k_4
G	$(A + C)$	k_5
DE	$(A + B + C)$	k_6

Divisor selection

Kernels are often good divisors, extract and substitute

$$L = AF + BF + AG + CG + ADE + BDE + CDE \quad 17 \text{ literals}$$

Divide by $k_6 = (A + B + C)$

$$L = AF + BF + AG + CG + DEk_6$$

Remaining kernels: $k_1 = (F + G)$, $k_4 = (A + B)$, $k_5 = (A + C)$

Pick one

$$L = Fk_4 + AG + CG + DEk_6$$

Divisor selection

$$L = Fk_4 + AG + CG + DEk_6$$

Remaining kernel: $k_5 = (A + C)$

$$L = Fk_4 + AG + CG + DEk_6$$

$$L = Fk_4 + Gk_5 + DEk_6$$

End result

$$L = F(A + B) + G(A + C) + DE(A + B + C) \quad 11 \text{ literals}$$

Node simplification

- During multi-level logic synthesis, representation broken into sub-functions
- Each sub-function (e.g., SOP form) needs to be minimized
$$L = AF + BF + AG + CG + ADE + BDE + CDE$$
- Similar to using Karnaugh Maps, Quine McCluskey, or Espresso to simplify expressions

$$\begin{aligned}L &= \bar{A} B + AC + BC \\ &= \bar{A} B + AC\end{aligned}$$

Node simplification

$F(A, B, C)$

		AB			
		00	01	11	10
C	0	0	1	0	0
	1	0	1	1	1

Node simplification

- Recall that two-level simplification can be improved using DON'T CARE information
- Need to find DON'T CARE automatically from Boolean network
- Take advantage of satisfiability DON'T CARES
 - Input can never occur
- Take advantage of observability DON'T CARES
 - Output is ignored for certain inputs

Outline

1. Multilevel minimization
2. Timing

Section outline

2. Timing

Delay models

Thresholds, noise, and debouncing

Hazards

Delay models




B



time

Delay models

 

Delay models



B



time

Delay models



Delay models




B



time

Delay models

 

Delay models




B



time

Delay models

 

Delay models



B



time

Delay models

- Ideal – No delay, outputs respond instantly to inputs
- Transport – Output shifted by some fixed duration
 - All input changes reflected at output

Delay models

- Inertial – Transitions that are not stable for more than some threshold period of time are absorbed by the gate
 - Provides a coarse approximation to real digital logic gate behavior
- Real – Outputs quickly respond to input changes
 - However, output changes have limited slew-rates


RC delay

- What happens when a transistor drives another transistor?
- Recall how CMOS transistors work


IO thresholds




IO thresholds

 


IO thresholds

 


IO thresholds

 


IO thresholds

 


IO thresholds

 


IO thresholds

 

IO thresholds

 

IO thresholds

 

Section outline

2. Timing

Delay models

Thresholds, noise, and debouncing

Hazards


IO thresholds

- *Digital* is a simplifying concept in a (macroscopically) *analog* world
- To treat signals as digital, need to define a dividing line between false and true
- What actually happens to the next stage when the voltage is at that line?
 - NMOS $V_{GS} > V_T$
 - PMOS $V_{GS} < -V_T$


IO thresholds

- *Digital* is a simplifying concept in a (macroscopically) *analog* world
- To treat signals as digital, need to define a dividing line between false and true
- What actually happens to the next stage when the voltage is at that line?
 - NMOS $V_{GS} > V_T$
 - PMOS $V_{GS} < -V_T$


Molten transistor

 


Molten transistor

 


Molten transistor

 


Molten transistor

 

Molten transistor

 

Molten transistor

 

IO thresholds

- Define valid ranges of logic high and logic low signals
- Undefined signals considered invalid

IO thresholds

- Better – However, still have a problem
- What happens if the output of a gate is near that threshold?
- Slight variation between gates might result in crossing this threshold for next gate
- How to compensate?
- Use separate input and output thresholds


IO thresholds

- Better – However, still have a problem
- What happens if the output of a gate is near that threshold?
- Slight variation between gates might result in crossing this threshold for next gate
- How to compensate?
- Use separate input and output thresholds


Separate IO thresholds

- Now, we can safely treat the system as digital
- However, digital systems talk with analog systems
- It is necessary to deal with noisy signals
- Real slew isn't ideal


Schmitt triggers

 


Schmitt triggers

 


Schmitt triggers

 

Schmitt triggers

 


Schmitt triggers

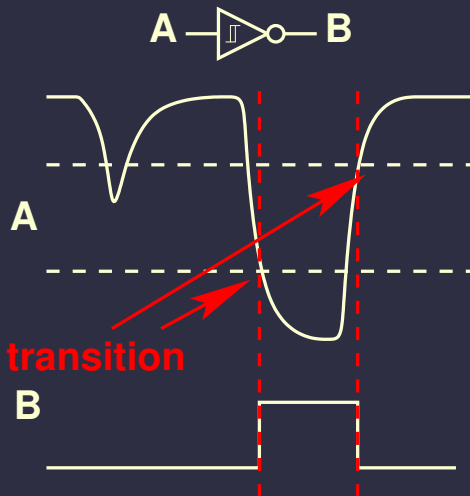


Reason for gradual transition

- A logic stage is an RC network
- Whenever a transition occurs, capacitance is driven through resistance
- Consider the implementation of a CMOS inverter



CMOS NOT is RC network

 



CMOS NOT is RC network

 


CMOS NOT is RC network

  



CMOS NOT is RC network

  


CMOS NOT is RC network

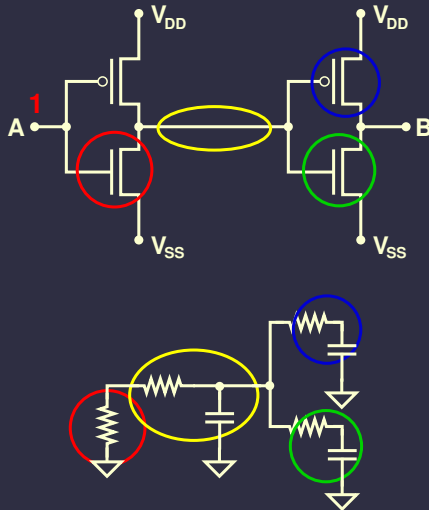

CMOS NOT is RC network

  


What is driven in NAND2?

 

Debouncing

- Mechanical switches bounce!
- What happens if multiple pulses?
 - Multiple state transitions
- Need to clean up signal

Debouncing

 

Improving device delay

- Decrease driven resistance and load
 - Use smaller transistors
 - Use shorter wire
 - Use wider wire (can increase load)

Improving device delay

- Increase drive by increasing width of driving transistors
 - Causes problems
 - Larger transistors provide larger loads to their inputs
 - In general, keep transistors small unless they absolutely need to drive large loads

Driving large loads

- Sometimes large loads need to be driven
- Long wires
- Output pads
- What happens if we go from a minimum-size inverter to a huge inverter?
 - Huge delay driving huge inverter's gate

Driving large loads

- Sometimes large loads need to be driven
- Long wires
- Output pads
- What happens if we go from a minimum-size inverter to a huge inverter?
 - Huge delay driving huge inverter's gate

Tapered buffer chain

- Instead, gradually increase buffers in chain
- Optimal number of stages: $\ln(C_{BIG}/C_{SMALL})$
- Stage width exponentially increases in α

$$W_1 = W_{MIN} \cdot \alpha^0$$

$$W_2 = W_{MIN} \cdot \alpha^1$$

$$W_3 = W_{MIN} \cdot \alpha^2$$

...


Useful delay: Debouncing

- Mechanical switches bounce
 - Noisy transition
- Use RC delay network to decrease transition speed
- Convert multiple noisy to single smooth transition
- Use Schmitt trigger to clean signal


Delay estimation in multi-level circuits

- Can get delay for a gate by knowing its drive (resistance) and the load it drives (RC)
 - Gate libraries will have this information
- Still need to get network delay
- Conduct topological sort of network to find earliest start times (EST)
- Always visit a node's parent before visiting it
- EST is maximum any parent's EST plus its delay


Topological sort

 


Topological sort

 


Topological sort

 


Topological sort

 


Topological sort

 


Topological sort

 


Topological sort

 


Topological sort

 


Topological sort

 


Topological sort

 

Topological sort

 



Topological sort

 

Slack


- Can use reverse topological sort from end nodes (given some target delay) to get latest start time (LST)
- Subtract delays and take minimum over children instead of adding delays and taking maximum over parents
- Subtract EST from LST to get node slack
- Gates with lowest slack are on critical path
- Make this path faster. . .
- . . . or save area (at the expense of speed) on non-critical paths

Useful delay: Rising edge pulse shaping

  

 Problem: Pulse width poorly controlled

Useful delay: Pulse rising/falling edge pulse shaping



Problem: Pulse width poorly controlled

Section outline

2. Timing

Delay models

Thresholds, noise, and debouncing


Hazards

Dynamic hazards

- Potential for two or more spurious transitions before intended transition
- Results from uneven path delays in some multi-level circuits



Dynamic hazards

 


Eliminating dynamic hazards

- Some approaches allow preservation of multi-level structure
 - Quite complicated to apply
- Simpler solution – Convert to two-level implementation

Static hazards


 
- Still have static hazards
- Potential for transient change of output to incorrect value



Problems with glitches

- These transitions result in incorrect output values at some times
- Also result in uselessly charging and discharging wire and gate capacitances through wire, gate, and channel resistances
 - Increase power consumption


Glitches increase power consumption

  


Detecting hazards

- The observable effect of a hazard is a glitch
 - A circuit that might exhibit a glitch has a hazard
- Whether or not a hazard is observed as a glitch depends on relative gate delays
- Relative gate delays change depending on a number of factors – Conditions during fabrication, temperature, age, etc.
- Best to use abstract reasoning to determine whether hazards might be observed in practice, under some conditions

Eliminating static hazards

 


input change within product term

 


$$F = \bar{A} D + A \bar{C}$$

Eliminating static hazards

 


input change within product term

 


$$F = \bar{A} D + A \bar{C}$$


Eliminating static hazards

 

ABCD = 1101

 

ABCD = 0101 (\bar{A} is still 0)

 

ABCD = 0101 (\bar{A} is 1)

Eliminating static hazards

- Add redundant primes covering all 1-1 transitions in SOP
- Add redundant primes covering all 0-0 transitions in POS
- Clearly primes can be used, consider contradiction stemming from assumption that non-prime is necessary to cover a transition

Where do static hazards really come from?

- Static-0: $A \bar{A}$
- Static-1: $A + \bar{A}$
- Assume SOP form has no product terms containing a variable in complemented and uncomplemented forms
 - Reasonable assumption, if true, drop product term

Where do static hazards really come from?

- Assume POS form has no sum terms containing a variable in complemented and uncomplemented forms
 - Reasonable assumption, if true, drop sum term
- Assume only one input switches at a time
- Conclusion: SOP has no 0-hazards and POS has no 1-hazards
 - In other words, if you are doing two-level design, you need not analyze the other form for hazards

Living with hazards

Sometimes hazards can be tolerated

- Combinational logic whose outputs aren't observed at all times
- Synchronous systems
- Systems without tight power consumption limits

Summary

- Brief review of cascaded carry lookahead adder
- Common ALU operations
- Overview of memory types
- Timing behavior