

Advanced Digital Logic Design – EECS 303

<http://ziyang.eecs.northwestern.edu/eeecs303/>

Teacher: Robert Dick
 Office: L477 Tech
 Email: dickrp@northwestern.edu
 Phone: 847-467-2298




**NORTHWESTERN
UNIVERSITY**

- Specification
- State diagram for FSM
- State table
- State minimization
- State assignment
- Derive state variable and output functions
- Simplify and implement the functions

- Design a vending machine controller that will release (output signal r) an apple as soon as 30¢ have been inserted
- The machine's sensors will clock your controller when an event occurs. The machine accepts only dimes (input signal d) and quarters (input signal q) and does not give change
- When an apple is removed from the open machine, it indicates this by clocking the controller with an input of d
- The sensors use only a single bit to communicate with the controller

- Sometimes, system specified in way that naturally maps to FSM
- Sometimes, path from specification to FSM is unclear
- Transform the specifications so they can naturally be represented as FSMs
 - E.g., regular expression \rightarrow NFA \rightarrow DFA \rightarrow FSM
- It's fine to go directly to FSM
 - Use transformations when they help you

$$0(0(0 + 1) + 1) + 1(0 + 1)$$

 

- 1 Construct implication chart, one square for each combination of states taken two at a time.
- 2 Square labeled S_i, S_j , if outputs differ than square gets X (0). Otherwise write down implied state pairs for all input combinations.
- 3 Advance through chart top-to-bottom and left-to-right. If square S_i, S_j contains next state pair S_m, S_n and that pair labels a square already labeled X (0), then S_i, S_j is labeled X (0).
- 4 Continue executing Step 3 until no new squares are marked with X (0).
- 5 For each remaining unmarked square S_i, S_j , then S_i and S_j are equivalent.

- We can enumerate the inputs on which an apple should be released
- $$ddd + ddq + dq + qd + qq$$
- $$d(dd + dq + q) + q(d + q)$$
- $$d(d(d + q) + q) + q(d + q)$$
- For $d, i = 0$, for $q, i = 1$
- $$0(0(0 + 1) + 1) + 1(0 + 1)$$

current state	next state		output (r)
	$i=0$	$i=1$	
A	B	E	0
B	C	D	0
C	D	D	0
D	A	A	1
E	D	D	0

B	BC, DE			
C	BD, DE	CD		
D	0	0	0	
E	BD, DE	CD	1	0
	A	B	C	D

D ≠ any other state

B	0			
C	0	0		
D	0	0	0	
E	0	0	1	0
	A	B	C	D

Easy – Merge C and E

- Incompletely specified machines are difficult to minimize
- Therefore, some merges can block others
- Need a formulation amenable to *backtracking*

	s'		
s	0	1	q
A	D	B	0
B	X	A	X
C	A	X	1
D	B	C	1

Consider merging A and B or B and C

- Assign values to states
- Keep state variable functions and output variable functions simple
- Allow cubes to be reused among different state variable functions

Assuming p states and k state variables

$$\frac{(2^k)!}{(2^k - p)!}$$
 possible assignments

Let's simplify that, assume p is an even power of two and

$$k = \lg_2 p$$

then,

$$2^k = p$$

Therefore, we have

$$\frac{p!}{(p-p)!} = \frac{p!}{0!} = p!/1 = p!$$
 possible assignments
$$p! \in \mathcal{O}(2^p)$$

- ... and that's a loose bound
- State assignment has a huge solution space
- It's also a hard problem

- Allow the extraction of common cubes for different state variable functions
 - State variables
 - States connected by transitions should be adjacent
 - Output functions
 - States with equivalent outputs should be adjacent
- Heuristic assignment popular
 - MUSTANG is popular
 - Attraction between states based on ability to extract common cubes

- Can do reasonably good state assignment by following guidelines. Make states have adjacent assignments (differing by only one bit) if:
- They have the same next (child) state in the state diagram for the same input
 - They have the same previous (parent) state in the state diagram
 - They have the same output for the same input


	00	01	11	10
0	A	C	E	G
1	B	D	F	H

- $a, b,$ and c are state variable bits
- $A, B, C,$ etc. are states
- State maps help select adjacent assignments for adjacent states

- States with same child for same input: $\{B, C\}$
- States with same parent: $\{B, C\}, \{C, D\}$
- States with same output: $\{A, B, C\}$
- Prioritize: $\{B, C\}, \{C, D\}, \{A, B, C\},$ etc.

current state	next state		output (r)
	$i=0$	$i=1$	
A	B	C	0
B	C	D	0
C	D	D	0
D	A	A	1

 - Recall that Karnaugh maps help us visualize adjacency
- Use state maps to visualize state adjacency
- Recall that we have n states, so we require $\lceil \lg_2(n) \rceil$ bit state variables
- $\lceil \lg_2(4) \rceil = 2$
- What if we hadn't done state minimization?
 - Five states \rightarrow three state variable bits required






	0	1
0	A	D
1	B	C



current state (jk)	next state (j^+k^+)		output (r)
	$i=0$	$i=1$	
00	01	11	0
01	11	10	0
11	10	10	0
10	00	00	1

Use Karnaugh maps (or other methods) to simplify functions

   - $j^+(j, k, i)$
- $k^+(j, k, i)$
- $r(j, k)$



  - Implement the state variable functions in combinational logic
- Use sequential elements along feedback paths
- Implement the output variable functions in combinational logic



- Can use advanced technique introduced in previous lecture
- Find the maximal compatibles
- Use these to generate the prime compatibles
- Write expression in POS form
- Multiply to get SOP form
- Formulate as a binate covering problem
- This technique is optimal but difficult
- State minimization for incompletely specified machines is a hard problem

	s ⁺			
s	0	1	q	
A	D	B	0	
B	X	A	X	
C	A	X	1	
D	B	C	1	

B	1		
C	0	1	
D	0	0	AB
	A	B	C

From Hachtel and Somenzi's Logic Synthesis and Verification Algorithms

B	1		
C	0	1	
D	0	0	AB
	A	B	C

{C, D}, {B, C}, {A, B}

B	1		
C	0	1	
D	0	0	AB
	A	B	C

A, B
B, C
C, D
D

AB

$$\{C, D\} \rightarrow \{A, B\}$$

$$\overline{\{C, D\}} + \{A, B\}$$

- {A, B} need to include A
- ({A, B} + {B, C}) need to include B
- ({B, C} + {C, D}) need to include C
- ({C, D} + {D}) need to include D
- ({C, D} + {A, B}) {C, D} class set requirements

- Choosing the compatible state sets is not straight-forward
- Some combinations block potential future combinations
- Know conflicting states from the compatibility table

- The combination of a pair of states may require the combination of another state pair
- Thus, using the maximal compatibles is insufficient
- Need additional prime compatibles that have smaller class sets
- Starting from the maximal compatibles, which are primes, generate other primes
- In order of decreasing compatible size, if the compatible has a non-empty class set, enter all subsets that are not already contained in other prime compatibles with empty class sets in the table

Once the prime compatibles are known, it is necessary to select a subset that

- Has minimal number of selected prime compatibles
- Covers all states
 - Would be unate covering
- Contains all class sets implied by the selected prime compatibles
 - This makes it binate covering
- Recall unate covering, similar solution works
 - Branch and bound

$$J_1 = \{A, B\}$$

$$J_2 = (\{A, B\} + \{B, C\})$$

$$J_3 = (\{B, C\} + \{C, D\})$$

$$J_4 = (\{C, D\} + \{D\})$$

$$J_5 = (\overline{\{C, D\}} + \{A, B\})$$

term	prime compatible				
	A, B	B, C	C, D	D	
J ₁	1				
J ₂	1	1			
J ₃		1	1		
J ₄			1	1	
J ₅	1		0		

Binate covering

term	prime compatible			
	A, B	B, C	C, D	D
J_1	1			
J_2	1	1		
J_3		1	1	
J_4			1	1
J_5	1		0	

- Find a set of columns, S , such that, for every row
 - A 1-column in the row is in S or...
 - ... a 0-column in the row is not in S

47

Robert Dick

Advanced Digital Logic Design

Today's Topics

- FSM design example (trying to use more examples)
- State minimization with don't-cares

49

Robert Dick

Advanced Digital Logic Design

Recommended reading

- <http://www.deepchip.com/gadfly/gad040703.html>
- <http://www.deepchip.com/gadfly/gad042803.html>
- Jayaram Bhasker. *A VHDL Primer*. Prentice-Hall, NJ, 1992
- Chapter 1
- Chapter 2

52

Robert Dick

Advanced Digital Logic Design

Additional examples

CS	NS(I)		Out
	0	1	
A	A	C	0
B	B	B	X
C	A	C	1

48

Robert Dick

Advanced Digital Logic Design

General CAD references

If you will be working in digital circuit design, bookmark these sites

- <http://www.deepchip.com>
 - Designers talk about the current state of CAD and circuit design
- <http://www.eetimes.com>
 - Electronics design trade journal
 - Won't find current research
 - Will find industry trends

50

Robert Dick

Advanced Digital Logic Design

Next lecture

- Design representations
- VHDL for combinational and sequential systems

53

Robert Dick

Advanced Digital Logic Design