


Advanced Digital Logic Design – EECS 303

<http://ziyang.eecs.northwestern.edu/eecs303/>

Teacher: Robert Dick
 Office: L477 Tech
 Email: dickrp@northwestern.edu
 Phone: 847-467-2298



NORTHWESTERN UNIVERSITY

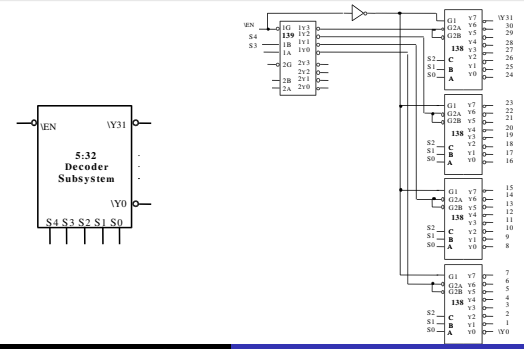


- Why is G1 connected to an inverted active-low enable signal?
- Why are 2A, 2B, and 2G not connected on the 74139 part?
- What would happen if this design were used and the parts were TTL (I don't expect you to know this one already)?
- How about CMOS?

- Given n -input circuit
- Count number of 1s in input

I_1	Zero	One
0	1	0
1	0	1


I_1	Zero	One
0	1	0
1	0	1

Can implement using logic gates

 



I_1	Zero	One
0	1	0
1	0	1

Can implement using TGs

 


I_1	Zero	One
0	1	0
1	0	1

Can implement using TGs

  


TG tally circuit

 


4-input tally

i_1	i_2	Zero	One	Two
0	0	1	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1

 

TG tally circuit

 


ROMs, FPGAs, and multi-level minimization

- Programmable read-only memories (PROMs)
- Field-programmable gate arrays (FPGAs)
- Programmable devices for prototyping


4-input tally

i_1	i_2	Zero	One	Two
0	0	1	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1

 


4-input tally

i_1	i_2	Zero	One	Two
0	0	1	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1

 


TG tally circuit

 

Programmable read-only memories (PROMs)

- 2-D array of binary values
- Input: Address
- Output: Word

PROM

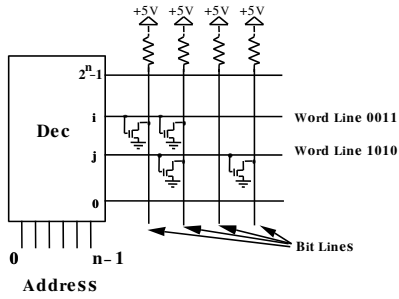


Truth table

A	B	C	F ₃	F ₂	F ₁	F ₀
0	0	0	0	1	0	0
0	0	1	0	1	1	1
0	1	0	0	0	1	0
0	1	1	1	0	0	0
1	0	0	1	1	0	1
1	0	1	0	0	0	1
1	1	0	1	0	0	0
1	1	1	0	0	1	0

Address Word

Memory composition

 

PLA/PAL vs. PROM

- PLA**
- Takes advantage of don't-cares
 - Good at random logic
 - Good when product terms shared
- PAL**
- More area-efficient for certain designs
 - OR-plane can't be programmed, usually no sharing

Implementing logic with PROMs


$$F_0 = \bar{A} \bar{B} C + A \bar{B} \bar{C} + A \bar{B} C$$

$$F_1 = \bar{A} \bar{B} C + \bar{A} B \bar{C} + A B C$$


$$F_2 = \bar{A} \bar{B} \bar{C} + \bar{A} B C + A \bar{B} \bar{C}$$

$$F_3 = \bar{A} B C + A \bar{B} \bar{C} + A B \bar{C}$$

PROM suitable for implementing example

 

Memory composition

 

Chip select

PLA/PAL vs. PROM


- PROM**
- Design trivial
 - Can't take advantage of don't-cares
 - Area-inefficient
 - Product/sum terms not shared

Field-programmable gate arrays (FPGAs)


- PLAs
 - 10–100 gate equivalent
- FPGAs
 - Altera
 - Actel
 - Xilinx
 - 100–1,000,000 gate equivalent

Altera erasable programmable logic devices (EPLDs)

 
Composed of many *macrocells* – 8 product term AND/OR array with programmable MUXs



Multiple array matrix (MAX)

 

MAX expander terms

 

Expander product terms shared among all macrocells


Altera EPLDs

- Each has from 8–48 macrocells
- Macrocell behavior controlled with EPROM bits
- Can be used sequentially
- Has synchronous and asynchronous modes


Multiple array matrix (MAX)

- Altera macrocells quite limited
 - Can't share product terms between macrocells
- Workaround: Connect together macrocells with programmable interconnect

MAX expander terms

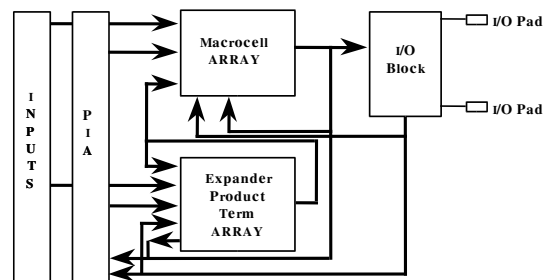

Altera 22V10 PAL

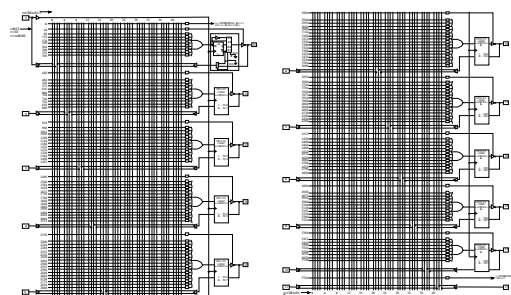


Altera 22V10 PAL

- Many product terms per output
- Latches and MUXs associated with outputs
- 22 IO pins
- 10 may be used as outputs

Actel programmable gate arrays


- Each combinational logic block has 8 inputs, 1 output
- No built-in sequential elements
- Build flip-flops using logic blocks

Actel logic block

 

Cross-couple for sequential use


Actel interconnect

 


Actel programmable gate arrays

- Rows of programmable logic blocks
- Rows of interconnect
- Columns of interconnect
- Attach to rows using antifuses


Actel logic block

 


Actel programmable gate arrays

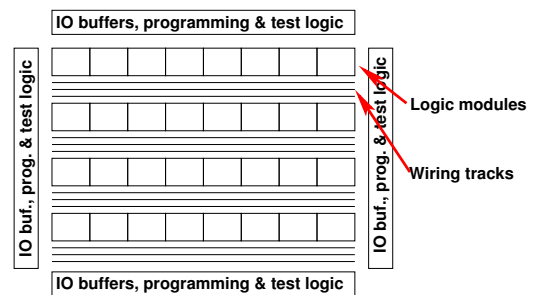

Antifuse routing

 

Actel routing example

 

- Minimize number of antifuse hops for critical path
- 2-3 hops for most interconnections

Xilinx LCA components


- Configurable logic blocks (CLBs)
- IO blocks (IOBs)
- Wiring channels

Xilinx LCA features

Inputs

- Input variables
- Tri-state (high-Z) enable bit for output
- Output clocks


Xilinx LCA

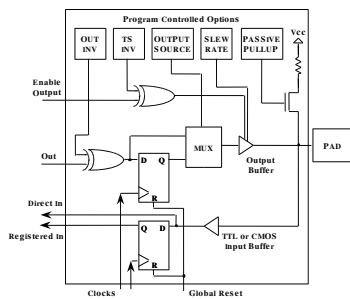

Xilinx logic cell arrays (LCAs)

- CMOS static RAM
 - Run-time programmable
- Serial shift-register based programming
- Program on power-up (external PROM)

Xilinx LCAs

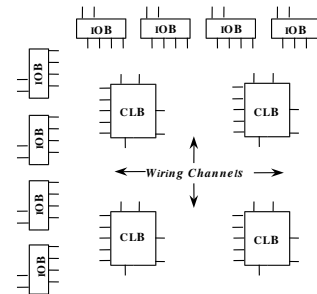


Xilinx LCA features

- Output the input bit
- Contains internal flip-flops for inputs and outputs
- Fast and slow outputs available, e.g., 5 ns vs. 30 ns
 - Slower option limits slew rate
 - Lower noise
 - Lower power consumption


Xilinx CLB

- 2 flip-flops
- General function of 4 variables
- 2 non-general functions of 5 variables
- Certain special-case functions of 6 variables
- Global reset
- Clock
- Clock enable
- Independent input, DIN

Xilinx CLB

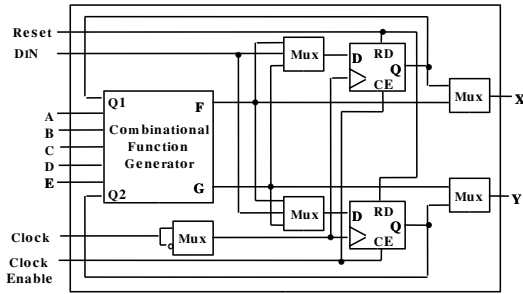

Function generator

 


Two arbitrary functions of four variables

PARITY5 CLB cost example


- Determine whether the number of 1s is even or odd
- $F = A \oplus B \oplus C \oplus D \oplus E$
- Implement using 1 CLB

Majority CLB cost example

 High whenever $\lceil n/2 \rceil$ outputs are high




Function generator

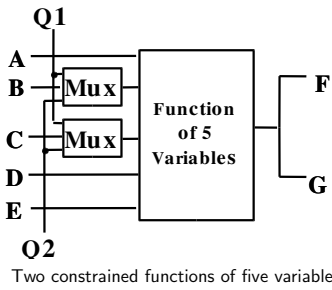

Two constrained functions of five variables

Function generator

 

Certain limited functions of 6 variables

2-bit comparator CLB cost example

$$A B = C D \text{ or } A B > C D$$


$$GT = A \bar{C} + A B \bar{D} + B \bar{C} \bar{D}$$

$$EQ = \bar{A} \bar{B} \bar{C} \bar{D} + \bar{A} B \bar{C} D + A \bar{B} C \bar{D} + A B C D$$

Only 1 CLB required


Large parity CLB cost example

2 levels allow up to 25 inputs

 

4-bit adder CLB cost example

 
Full adder, 4 CLB delays to final carry out (CO), 4 CLBs



Xilinx interconnect

- Short direct connections
- Global long lines
- Horizontal/vertical long lines
- Switching matrix connections

Xilinx interconnect

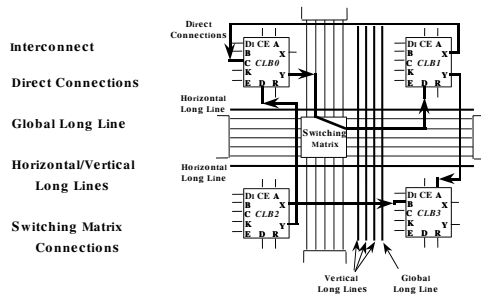


Dynamic reconfiguration

- Serial configuration slow
 - Parallelize
- Full reconfiguration slow
 - Partial reconfiguration
- Reconfiguration slow
 - Use configuration cache

4-bit adder CLB cost example

 Composition from 2 2-bit adders give 2 CLB delay, 6 CLB cost



Xilinx interconnect

- Hierarchical routing organization
- Some designs are constrained by routing resources
- Can use logic CLBs to control routing
- Substantial communication power consumption

Example Xilinx parts

Parameter	XC4024	XC3195	XC2018
Number of FFs	2,560	1,320	174
Number of IOs	256	176	74
Number of logic inputs per CLB	9	5	4
Function generators per CLB	3	2	2
Fast carry logic	yes	no	no
Number of logic outputs per CLB	4	2	2
RAM bits	32,768	0	0

FPGA application examples

- Prototyping
- Constant coefficient multiplication
- Direct HW implementation of problem instance, e.g.,
 - 3SAT
 - Design rule checking (DRC)

Prototype designs

- Discrete packages
 - Slow
 - Error-prone
- Custom layout requires circuit fabrication
 - Slow
 - Expensive for small runs
 - Can't be changed

70

Robert Dick

Advanced Digital Logic Design

Programmable devices in prototyping

- Programmable read-only memories (PROMs)
 - Inefficient for implementing random logic
 - Write-once
- Erasable programmable read-only memories (EPROMs)
 - Can be erased
 - Erasure slow (UV)
 - Expensive package window

72

Robert Dick

Advanced Digital Logic Design

DeMorgan's Law for CMOS

$$\begin{aligned}\overline{(A+B)} &= \bar{A} \bar{B} \\ \overline{(AB)} &= \bar{A} + \bar{B} \\ A + B &= \overline{\bar{A} \bar{B}} \\ AB &= \overline{\bar{A} + \bar{B}}\end{aligned}$$

75

Robert Dick

Advanced Digital Logic Design

DeMorgan's Law for OR/NAND

A	\bar{A}	B	\bar{B}	A + B	$\overline{(\bar{A} \bar{B})}$	$\bar{A} + \bar{B}$	(AB)
0	1	0	1	0	0	1	1
0	1	1	0	1	1	1	1
1	0	0	1	1	1	1	1
1	0	1	0	1	1	0	0

77

Robert Dick

Advanced Digital Logic Design

Programmable devices in prototyping

- Multiplexers (MUXs) and demultiplexers (DMUXs)
 - Wiring them up is tedious and error-prone
- Programmable array logic (PAL) and programmable logic array (PLA)
 - Fuses blown, write-once
- Generic array logic (GAL)
 - Electrically reprogrammable

71

Robert Dick

Advanced Digital Logic Design

Programmable devices in prototyping

- Electrically erasable programmable read-only memories (EEPROMs)
 - Erasure fast
 - Packaging less expensive
 - Potential for in-circuit erasure
- Field-programmable gate arrays (FPGAs) are ideal
 - If market size small, ship FPGAs
- In-circuit programming practical

73

Robert Dick

Advanced Digital Logic Design

DeMorgan's Law for CMOS

- OR is the same as NAND with complemented inputs
- AND is the same as NOR with complemented inputs
- NAND is the same as OR with complemented inputs
- NOR is the same as AND with complemented inputs

76

Robert Dick

Advanced Digital Logic Design

DeMorgan's Law for AND/NOR


A	\bar{A}	B	\bar{B}	AB	$\overline{(\bar{A} + \bar{B})}$	$\bar{A} \bar{B}$	(A + B)
0	1	0	1	0	0	1	1
0	1	1	0	0	0	0	0
1	0	0	1	0	0	0	0
1	0	1	0	1	1	0	0

78


Robert Dick

Advanced Digital Logic Design


AND/OR → NAND/NOR

 

AND/OR → NAND/NOR

 


AND/OR/NOT network to NAND/NOR

 


Review

- Two-level transformations and minimization
- Multi-level minimization
- Design with various implementation technologies

AND/OR → NAND/NOR

 

AND/OR → NAND/NOR

 

Homework

Review for midterm exam on Thursday

Will post solutions to homework tonight

Responsible for all reading, assignments, labs