

EECS 312: Digital Integrated Circuits
Midterm Exam

2 December 2010

Robert Dick

Show your work. Derivations are required for credit; end results are insufficient.
Closed book. No electronic mental aids, e.g., calculators.

Honor Pledge: I have neither given nor received aid in this exam.

Signature:

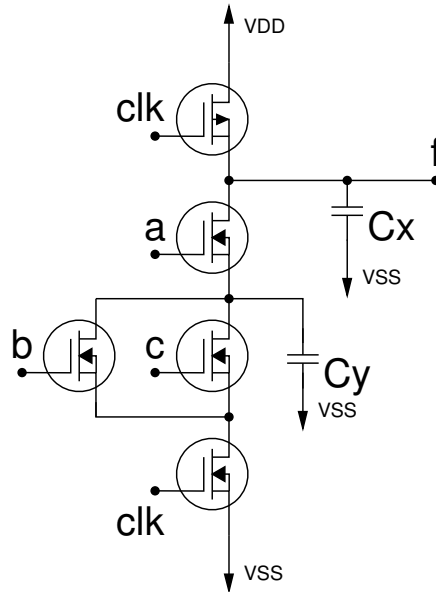


Figure 1: Example circuit.

1. **(20 pts.)** Consider the circuit in Figure 1. Hint: The top transistor is a PMOSFET and the rest are NMOSFETs.
 - (a) **(1 pts.)** What style of logic is this implemented in?
 - (b) **(1 pts.)** Is this an example of ratioed logic?
 - (c) **(5 pts.)** What function is implemented?
 - (d) **(8 pts.)** If $C_x = 5C_Y$, then what is the lowest voltage node f may reach during the evaluate stage if a transitions from 0 V to 2.5 V but b and c remain at 0 V. Show your work. State and support your assumptions.

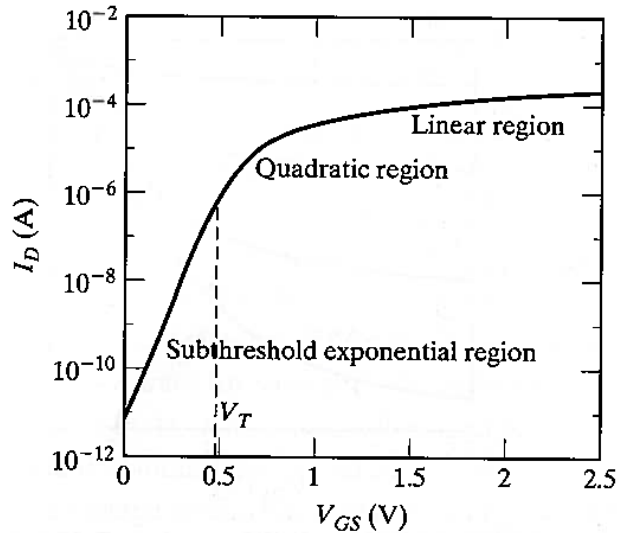


Figure 2: NMOSFET I_D - V_{GS} curve.

- (e) **(5 pts.)** If $clk, a, b,$ and c are all 0 V, V_{CY} is 0.25 V, and Figure 2 gives the I_D - V_{GS} curve for each NMOSFET, find an upper bound on the leakage current for the logic gate. Hint: It is fine to extrapolate.
2. **(10 pts.)** Consider a load with resistance R and capacitance C that is driven by a time-varying voltage source.
- (a) **(5 pts.)** Derive an expression for the total energy consumed in the resistor if the voltage source changes instantly from 0 V to 2.5 V at time zero.
- (b) **(5 pts.)** If the input voltage changes from 0 V to 2.5 V gradually instead of instantly, what is the effect on the total energy consumed in the resistor? Explain your answer. A correct but unsupported answer is not sufficient.
3. **(10 pts.)** Consider the circuit in Figure 3. V_s changes from 0 V to 2.5 V at time zero.
- (a) **(5 pts.)** Derive an expression for the time constant when driving node d .
- (b) **(5 pts.)** Derive an expression for the time at which V_d will reach 2 V. Hint: If you think you need a calculator, check the references at the end of the exam for a good alternative.
4. **(10 pts.)** Consider the layout in Figure 4.
- (a) **(2 pts.)** What type of logic function does this layout implement?
- (b) **(8 pts.)** Point out the three largest problems with this layout. For each explain the impact on gate behavior. When possible, indicate the ways in which important parameters are influenced, e.g., k' .
5. **(5 pts.)** Using three or fewer sentences, explain one difference in the requirements for 6T cell SRAM sense amplifiers and 1T cell DRAM sense amplifiers.

 


Figure 3: RC network.

 


Figure 4: Messed up layout.

6. (5 pts.) Using three or fewer sentences, explain what silicides are and why they are useful.
7. (5 pts.) Draw both a high-level symbol and transistor-level schematic for a falling-edge triggered flip-flop with two inputs, a and b . The output of the flip-flop should toggle if a is 2.5 V or b is equal to the current output of the flip-flop but should otherwise remain unchanged. If gate sizing is important, specify it. You may use hierarchy, i.e., once you show the structure of an inverter once and give a symbol for it, you may use the symbol from then on.
8. (5 pts.) Using three or fewer sentences, give an example of a situation in which it is important to consider interconnect parasitic inductance and explain a problem caused by this parasitic inductance.

1 Reference material

	C_{OX} (fF/ μm^2)	C_O (fF/ μm)	C_j (fF/ μm^2)	m_j	ϕ_b (V)	C_{jsw} (fF/ μm)	m_{jsw}	ϕ_{bsw} (V)
NMOS	6	0.31	2	0.5	0.9	0.28	0.44	0.9
PMOS	6	0.27	1.9	0.48	0.9	0.22	0.32	0.9

MODELS FOR CMOS DEVICES

CMOS (0.25 μm) – Unified Model.

	V_{T0} (V)	γ ($\text{V}^{0.5}$)	V_{DSAT} (V)	k' (A/V^2)	λ (V^{-1})
NMOS	0.43	0.4	0.63	115×10^{-6}	0.06
PMOS	-0.4	-0.4	-1	-30×10^{-6}	-0.1

CMOS (0.25 μm) – Switch Model (R_{eq})

V_{DD} (V)	1	1.5	2	2.5
NMOS (k Ω)	35	19	15	13
PMOS (k Ω)	115	55	38	31

CMOS (0.25 μm) – BSIM Model


See Website: <http://bwrc.eecs.berkeley.edu/IcBook>

Name	Value
kT/q	25.875 mJ/C
NMOSFET I_S	21.0 pA
PMOSFET I_S	41.8 pA
n (for I_D calculation)	1.5

VALUES OF MATERIAL AND PHYSICAL CONSTANTS

Name	Symbol	Value	Units
Room temperature	T	300 ($\approx 27^\circ\text{C}$)	K
Boltzman constant	k	1.38×10^{-23}	J/K
Electron charge	q	1.6×10^{-19}	C
Thermal voltage	$\phi_T = kT/q$	26	mV (at 300 K)
Intrinsic Carrier Concentration (Silicon)	n_i	1.5×10^{10}	cm^{-3} (at 300 K)
Permittivity of Si	ϵ_{Si}	1.05×10^{-12}	F/cm
Permittivity of SiO_2	ϵ_{SiO_2}	3.5×10^{-13}	F/cm
Resistivity of Al	ρ_{Al}	2.7×10^{-8}	$\Omega\text{-m}$
Resistivity of Cu	ρ_{Cu}	1.7×10^{-8}	$\Omega\text{-m}$
Magnetic permeability of vacuum (similar for SiO_2)	μ_0	12.6×10^{-7}	Wb/Am
Speed of light (in vacuum)	c_0	30	cm/nsec
Speed of light (in SiO_2)	c_{SiO_2}	15	cm/nsec

The natural logarithm of x

 

FORMULAS AND EQUATIONS

Diode

$$I_D = I_S(e^{V_D/\phi_T} - 1) = Q_D/\tau_T$$

$$C_j = \frac{C_{j0}}{(1 - V_D/\phi_0)^m}$$

$$K_{eq} = \frac{-\phi_0^m}{(V_{high} - V_{low})(1 - m)} \times \frac{1}{[(\phi_0 - V_{high})^{1-m} - (\phi_0 - V_{low})^{1-m}]}$$

MOS Transistor

$$V_T = V_{T0} + \gamma(\sqrt{|-2\phi_F + V_{SB}|} - \sqrt{|-2\phi_F|})$$

$$I_D = \frac{k_n W}{2 L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS}) \text{ (sat)}$$

$$I_D = v_{sat} C_{ox} W \left(V_{GS} - V_T - \frac{V_{DSAT}}{2} \right) (1 + \lambda V_{DS}) \text{ (velocity sat)}$$

$$I_D = k_n \frac{W}{L} (V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \text{ (triode)}$$

$$I_D = I_S e^{\frac{V_{GS}}{n k T / q}} \left(1 - e^{-\frac{V_{DS}}{k T / q}} \right) \text{ (subthreshold)}$$

Deep Submicron MOS Unified Model

$$I_D = 0 \text{ for } V_{GT} \leq 0$$

$$I_D = k' \frac{W}{L} \left(V_{GT} V_{min} - \frac{V_{min}^2}{2} \right) (1 + \lambda V_{DS}) \text{ for } V_{GT} \geq 0$$

$$\text{with } V_{min} = \min(V_{GT}, V_{DS}, V_{DSAT})$$

$$\text{and } V_{GT} = V_{GS} - V_T$$

MOS Switch Model

$$R_{eq} = \frac{1}{2} \left(\frac{V_{DD}}{I_{DSAT}(1 + \lambda V_{DD})} + \frac{V_{DD}/2}{I_{DSAT}(1 + \lambda V_{DD}/2)} \right) \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left(1 - \frac{5}{6} \lambda V_{DD} \right)$$

Inverter

$$V_{OH} = f(V_{OL})$$

$$V_{OL} = f(V_{OH})$$

$$V_M = f(V_M)$$

$$t_p = 0.69 R_{eq} C_L = \frac{C_L (V_{swing}/2)}{I_{avg}}$$

$$P_{dyn} = C_L V_{DD} V_{swing} f$$

$$P_{stat} = V_{DD} I_{DD}$$

Static CMOS Inverter

$$V_{OH} = V_{DD}$$

$$V_{OL} = GND$$

$$V_M \approx \frac{r V_{DD}}{1 + r} \text{ with } r = \frac{k_p V_{DSATp}}{k_n V_{DSATn}}$$

$$V_{IH} = V_M - \frac{V_M}{g} \quad V_{IL} = V_M + \frac{V_{DD} - V_M}{g}$$

$$\text{with } g \approx \frac{1 + r}{(V_M - V_{Tn} - V_{DSATn}/2)(\lambda_n - \lambda_p)}$$

$$t_p = \frac{t_{pHL} + t_{pLH}}{2} = 0.69 C_L \left(\frac{R_{eqn} + R_{eqp}}{2} \right)$$

$$P_{av} = C_L V_{DD}^2 f$$

Interconnect

$$\text{Lumped RC: } t_p = 0.69 RC$$

$$\text{Distributed RC: } t_p = 0.38 RC$$

RC-chain:

$$\tau_N = \sum_{i=1}^N R_i \sum_{j=i}^N C_j = \sum_{i=1}^N C_i \sum_{j=1}^i R_j$$

Transmission line reflection: , , ,

$$\rho = \frac{V_{refl}}{V_{inc}} = \frac{I_{refl}}{I_{inc}} = \frac{R - Z_0}{R + Z_0}$$

CMOS COMBINATIONAL LOGIC

Transistor Sizing using Logical Effort

$$F = \frac{C_L}{C_{g1}} = \prod_{i=1}^N \frac{f_i}{b_i} \quad G = \prod_{i=1}^N g_i \quad D = t_{p0} \sum_{j=1}^N \left(p_j + \frac{f_j g_j}{\gamma} \right)$$

$$B = \prod_{i=1}^N b_i \quad H = FGB \quad D_{min} = t_{p0} \left(\sum_{j=1}^N p_j + \frac{N(N/H)}{\gamma} \right)$$