

EECS 312 Discussion 2



09/13

Shengshuo Lu
(luss@umich.edu)


Overview

- Reminder
 - Lab 1: Due Sep 17
 - Special Topics Sign up sheet
 - VNC
- Logic Gates
- Power
- Diode

NMOS

  

Logic Gates

 


Inverter

Complementary CMOS



- Complementary CMOS logic gates
 - nMOS *pull-down network*
 - pMOS *pull-up network*
 - Also called static CMOS

	Pull-up OFF	Pull-up ON
Pull-down OFF	Z (float)	1
Pull-down ON	0	X (crowbar)

 



CMOS NAND Gate

A	B	Y	Z
0	0	1	$\sim 100\text{mV}$
0	1	1	0
1	0	1	$V_{DD} - V_{th}$
1	1	0	0

  

CMOS NOR Gate




A	B	Y	Z
0	0	1	1
0	1	0	1
1	0	0	V_{th}
1	1	0	$\sim V_{DD}-100mV$

  

Tristates


- *Tristate buffer* produces Z when not enabled

EN	A	Y
0	0	Z
0	1	Z
1	0	0
1	1	1

   


Tristate Inverter

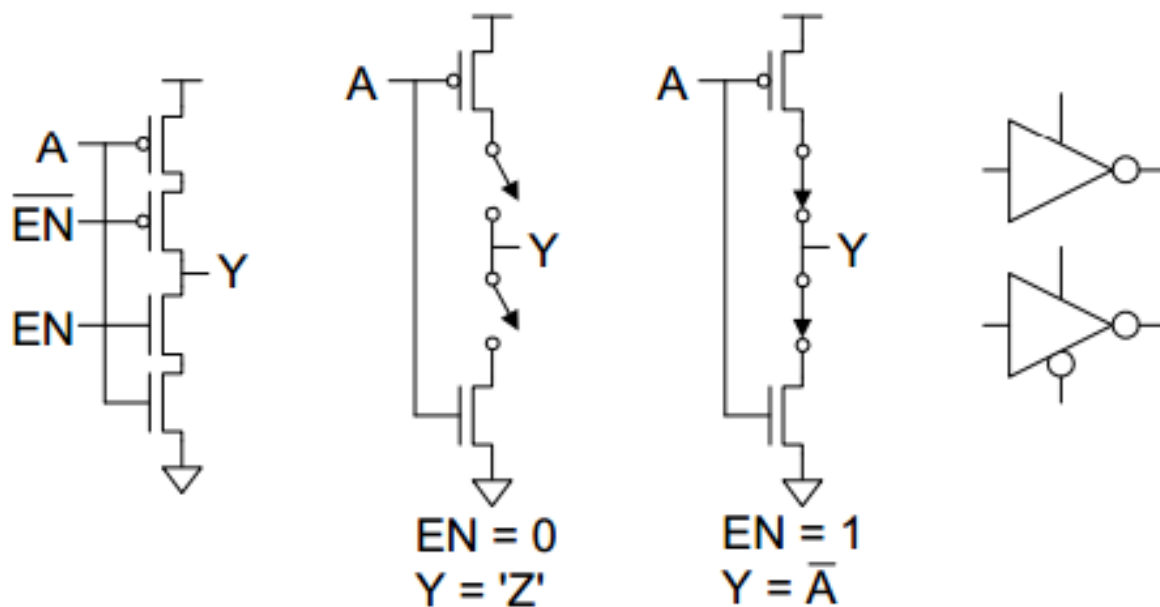- Tristate inverter produces restored output
 - Violates conduction complement rule
 - Because we want a Z output



Power

 - Dynamic Power
- Static Power
- Short-Circuit Power *



Power

$$P = P_{SWITCH} + P_{SHORT} + P_{LEAK}$$

$$P_{SWITCH} = C \cdot V_{DD}^2 \cdot f \cdot A$$

$$\dagger P_{SHORT} = \frac{b}{12} (V_{DD} - 2 \cdot V_T)^3 \cdot f \cdot A \cdot t$$

$$P_{LEAK} = V_{DD} \cdot (I_{SUB} + I_{GATE} + I_{JUNCTION} + I_{GIDL})$$

C : total switched capacitance

V_{DD} : high voltage

f : switching frequency

A : switching activity

b : MOS transistor gain

V_T : threshold voltage



t : rise/fall time of inputs

$\dagger P_{SHORT}$ usually $\leq 10\%$ of P_{SWITCH}


Smaller as $V_{DD} \rightarrow V_T$

$A < 0.5$ for combinational nodes, 1 for clocked nodes.

Diode

  


Diode

 


Diode

- Reverse Bias

 

- Forward Bias

 

Diode

