

EECS 312 Discussion 6



10/11

Shengshuo Lu
(luss@umich.edu)



Overview

- Reminder
 - Lab 3: Due Oct 25


CMOS Inverter

  


CMOS Inverter

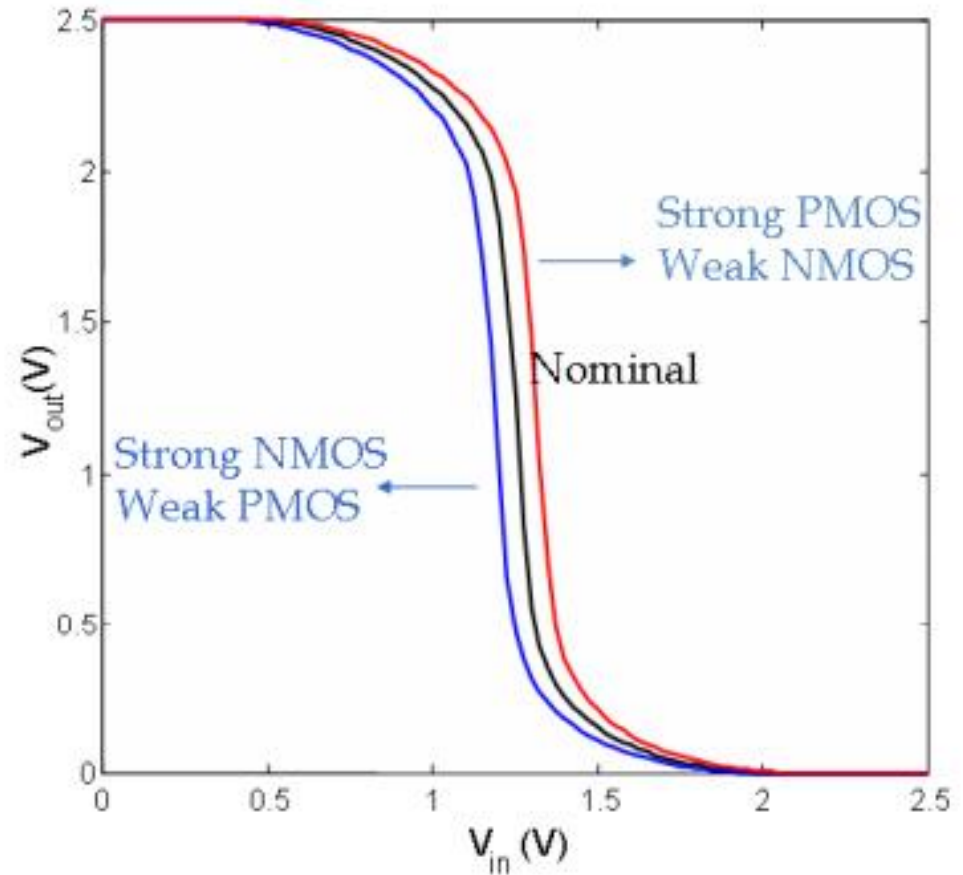 

Delay Definition

 

A First-Order RC Network

 


$$V_{out}(t) = (1 - e^{-t/\tau})V$$

$$\tau = R \times C$$

$$t_p = \ln(2)\tau = 0.69R \times C$$

CMOS Inverter: Transient Response

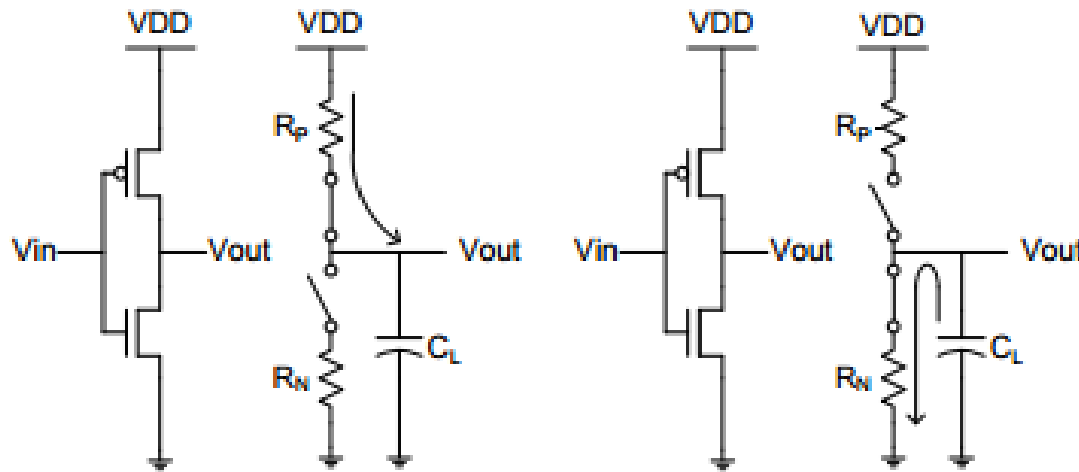

$$V_{in} = 0$$

(a) Low-to-high

$$V_{in} = V_{DD}$$

(b) High-to-low

$$t_{pHL} = f(R_N \times C_L)$$

$$t_{pHL} = 0.69 R_N \times C_L$$


$$t_{pLH} = 0.69 R_P \times C_L$$

Capacitance


- Any two conductors separated by an insulator have capacitance
- Gate to channel capacitor is very important
 - Creates channel charge necessary for operation
- Source and drain have capacitance to body
 - Across reverse-biased diodes
 - Called diffusion capacitance because it is associated with source/drain diffusion

Gate Capacitance

 - Gate capacitance can be complex, but we will use a simple model
- $C_{GC} = \epsilon_{ox} WL/t_{ox} = C_{ox} WL = C_{per_micron} W$





 SiO₂ gate oxide
(good insulator, $\epsilon_{ox} = 3.9\epsilon_0$)





Diffusion Capacitance

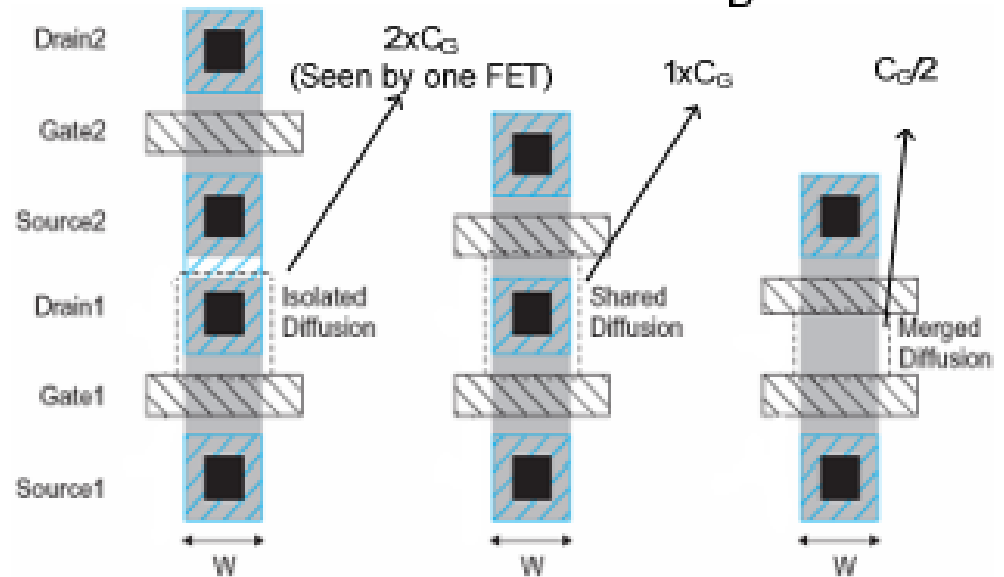 - C_{SB} , C_{DB}
- Undesirable, called *parasitic* capacitance
- Capacitance depends on area and perimeter
 - Use small diffusion nodes
 - Comparable to C_G for contacted diff
 - $\frac{1}{2} C_G$ for uncontacted
 - Varies with process



Diffusion Capacitance: Example

  
- Easiest to assume a contacted diffusion on every source/drain
- BUT: Good layout minimizes diffusion area
- Ex: NAND3 layout shares one diffusion contact
 - Reduces output capacitance by $2C$
 - Merged uncontacted diffusion helps also




Design for Performance

- Keep capacitances small – lower C
 - Compact layout, good placement (short wires & no diffusion routing)
- Increase transistor sizes – lower R
 - Watch out for self-loading! – parasitic C increases!
- Increase V_{DD}
 - Not usually possible due to reliability and power penalties

Device Sizing

 


$$S = W_p/W_{p_min} = W_n/W_{n_min}$$

 

Increasing device width
Leads to self-loading:
Intrinsic capacitances
dominate


Input Pattern Effects on Delay

 


- Delay is dependent on the **pattern** of inputs
- *Ignore C_{int} for the moment!*
- Low to high transition
 - both inputs go low
 - delay is $0.69 R_p/2 C_L$
 - one input goes low
 - delay is $0.69 R_p C_L$
- High to low transition
 - both inputs go high
 - delay is $0.69 2R_n C_L$

Fast Complex Gates: Design Techniques

- Transistor Ordering

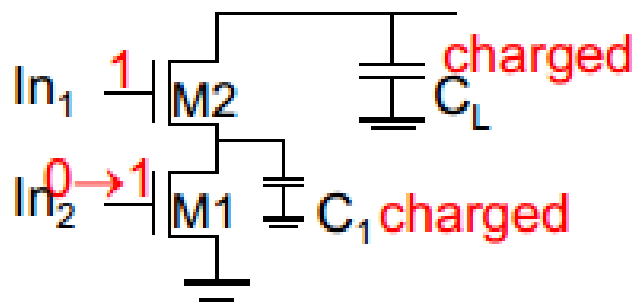


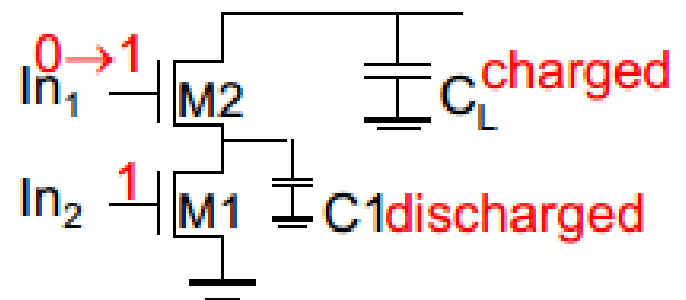delay determined by time to discharge C_L , C_1



delay determined by time to discharge C_L



Delay Dependence on Input Patterns

 


Input Data Pattern	Delay (psec)
A=B=0→1	69
A=1, B=0→1	62
A=0→1, B=1	50
A=B=1→0	35
A=1, B=1→0	76
A=1→0, B=1	57

NMOS = $0.5\mu\text{m}/0.25\mu\text{m}$
PMOS = $0.75\mu\text{m}/0.25\mu\text{m}$
 $C_L = 100\text{ fF}$

Transistor Sizing

  


Transistor Sizing a Complex CMOS Gate

 

$$\text{OUT} = \overline{D + A \cdot (B + C)}$$

Transistor Sizing a Complex CMOS Gate

 

$$\text{OUT} = D + A \cdot (B + C)$$

Summary

- CMOS delays dictated by device sizing, layout, wires
 - RC model is accurate to first-order
 - Computing delays of complex gates is challenging due to input pattern dependency
 - Watch out for self-loading; size appropriately

HW2 Q6

- V_t of A = $-0.4V$
- V_t of B = $0.4V$
- $V_{dd} = 2.5V$

