

# EECS 312 Discussion 9

11/1

Shengshuo Lu  
(luss@umich.edu)


# Overview

- Reminder
  - Lab 4: Due Nov 7
- Classic CMOS gate review
- DCVS (Differential Cascode Voltage Switch)
- Pass Gate Logic
- Dynamic Logic

# Static Logic Families

 
# Classic CMOS

- Advantages:
  - Non-ratioed
  - $\sim 0$  static power
  - Low S.C. power  $\sim 10\%$  of dynamic power
  - Full rail swing
  - Good noise margins
  - True and complement functions



 
# Classic CMOS


- Disadvantages:
  - Large # of transistors, large area
  - Slow
    - PMOS mobility
    - Transistor cap from dual function
  - Increasing static power due to leakage



Tradeoff

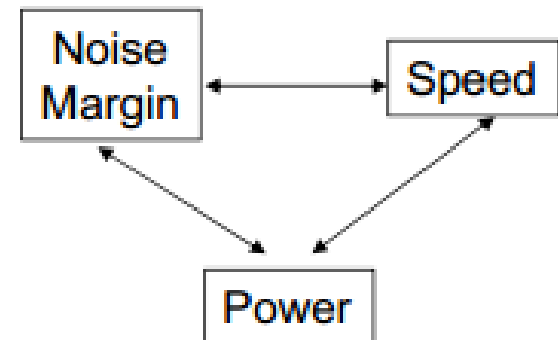

 
# Differential Cascode Voltage Switch DCVS




← PMOS stack with NMOS
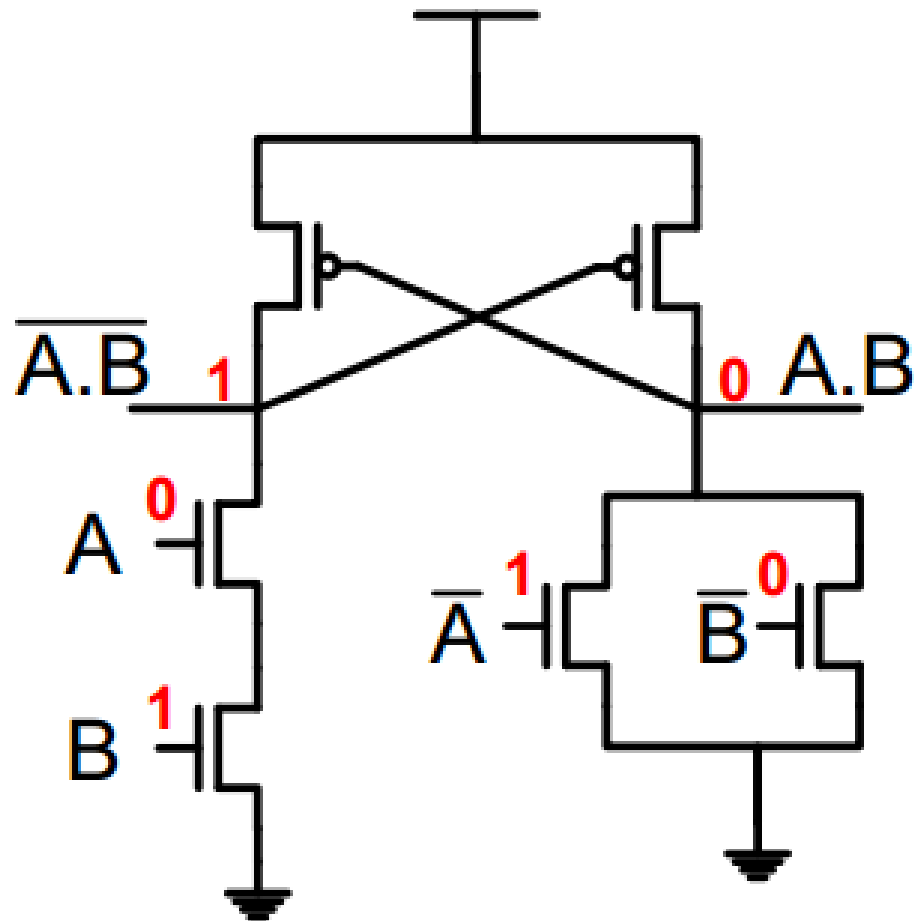
# Differential Cascode Voltage Switch DCVS



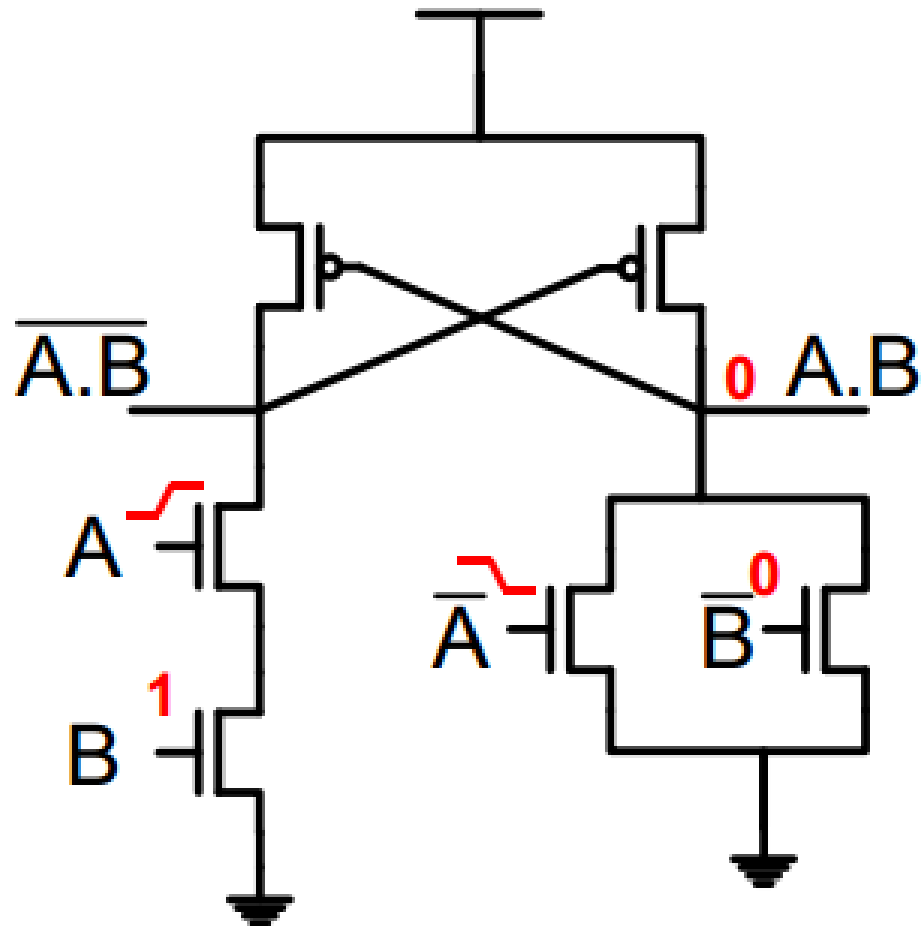
# Differential Cascode Voltage Switch DCVS





 
# Differential Cascode Voltage Switch DCVS



 
# Differential Cascode Voltage Switch DCVS




Timing of outputs:  
Which first?  
Q or Qbar
 
# Differential Cascode Voltage Switch DCVS




- Advantages:
  - No PMOS duality
    - Lower input cap.
    - Use only NMOS
  - Faster than CMOS
  - Can evaluate complex logic trees in 1 stage
 
# Differential Cascode Voltage Switch DCVS




- Disadvantages:
  - Need complementary inputs (dual rail)
  - Cross-bar current
    - Sensitive to input timing
  - Sizing of PMOS is hard
    - Too large  $\rightarrow$  PDN does not switch the output
    - Too small  $\rightarrow$  Slow rise time
- Ratioed Logic?

# Pass Gate Logic

 


- **Advantages:**
  - Speed: 20-50% faster (less capacitance)
    - In some circuits, such as XOR/MUX
  - Lower dynamic power

# Pass Gate Logic

 

- Disadvantages:
  - Very sensitive to noise: 2 types
    - $V_t$  drop  $\rightarrow$  must level restore someplace
    - Sensitive to undershoot voltage noise on inputs
      - Buffers at inputs suppresses this effect
  - Body effect  $\rightarrow$  limit # of FETs in series

# Pass Gate Logic

 


- Disadvantages:
  - Delay dependence on state
  - Cannot be cascaded without output inverter
  - Added leakage in output inverter

# Dynamic Logic Families




# Basic Domino gate

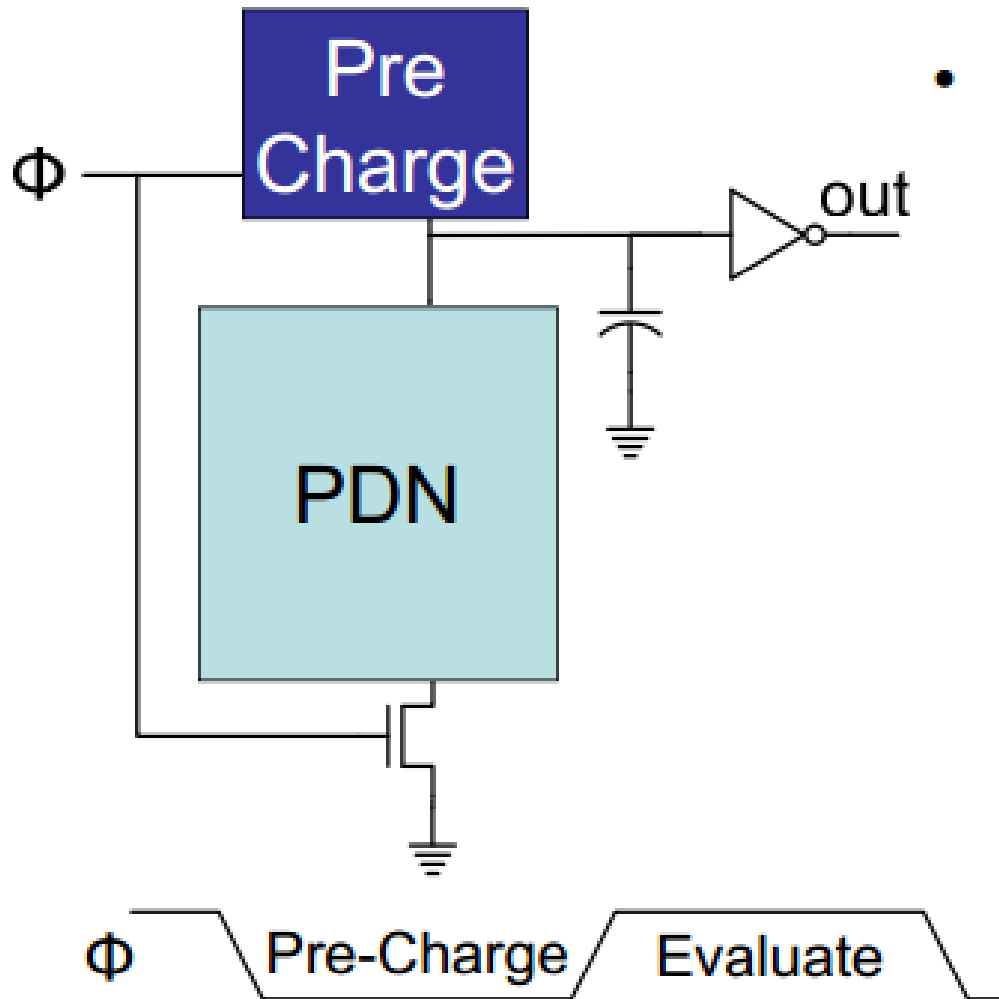


- Divide the clock in 2 phases:
  - Precharge
    - Output Low
    - Dyn. Cap precharge
    - PDN Off
  - Evaluate
    - Conditional discharge
    - Input must be stable and monotonic L $\rightarrow$ H

# Domino / Static $C_{in}/C_{out}$

3-input OR gate

 


Static:  
 $C_i = 7$   
 $C_n = 9$

 

Dynamic:  
 $C_i = 2$   
 $C_n = 7$


# Basic Domino gate

 

## • Advantages:

- Faster than CMOS
- Input capacitance is lower
- Early switch point
- Inverter  $P/N > 2$  (only rising delay important)


# Basic Domino gate

 

## Disadvantages:

- Low noise margin
- Charge sharing
- Leakage currents
- Internal capacitance charge sensitive to noise

# Issues: Leakage

 

- Dynamic node is floating during evaluation
  - Leakage current of NMOS can discharge it